


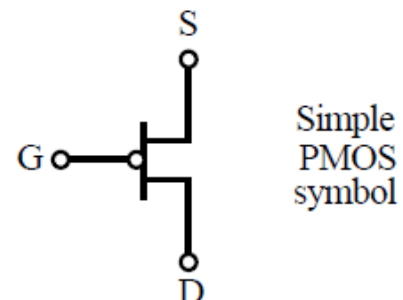
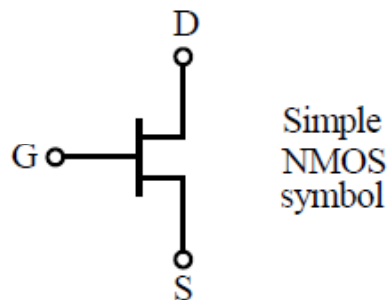
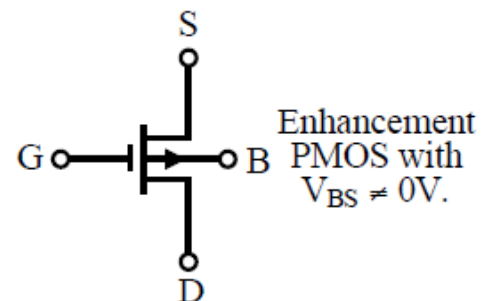
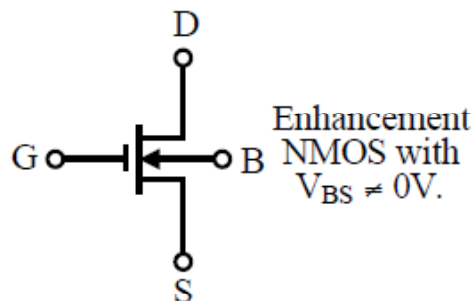


MOS Symbol:

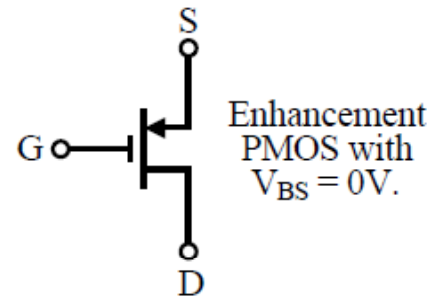

CMOS Process:

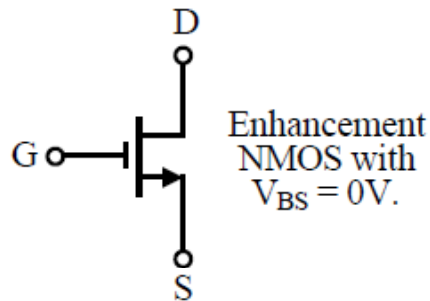

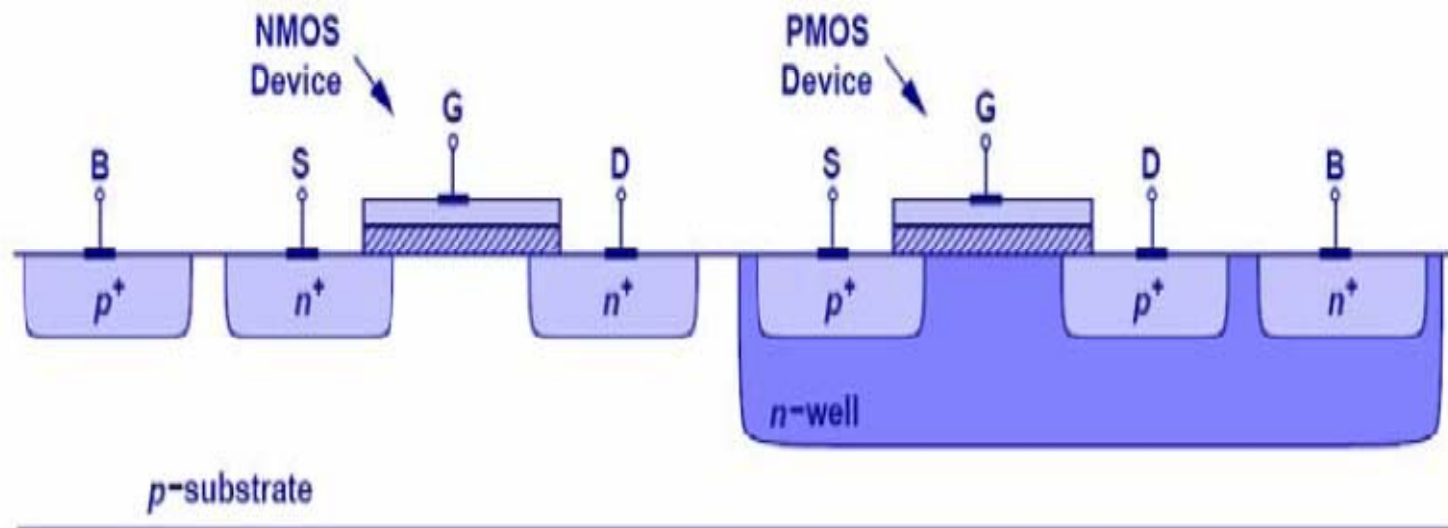

Simple MOS Large-Signal Model:

3 regions of operation:

Cutoff Region:

$$i_D = 0, V_{GS} - V_{TH} < 0 \text{ (ignores subthreshold current)}$$

Linear, Triode, or Non-saturation Region:

$$i_D = \frac{\mu_o C_{ox} W}{L} \left[(V_{GS} - V_{TH}) - \left(\frac{V_{DS}}{2} \right) \right] V_{DS}, 0 < V_{DS} < V_{GS} - V_{TH}$$

Active or Saturation Region:

$$i_D = \frac{\mu_o C_{ox} W}{2L} (V_{GS} - V_{TH})^2, 0 < V_{GS} - V_{TH} < V_{DS}$$


μ_o = surface mobility of the channel for the n-channel or p-channel device (cm²/Volt.Sec)

$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$ = capacitance per unit area of the gate oxide (F/cm²)

ϵ_{ox} = permittivity of SiO₂ = 3.9 * 8.854e-14 (F/cm)


t_{ox} = oxide thickness

Output Characteristic of NMOS:

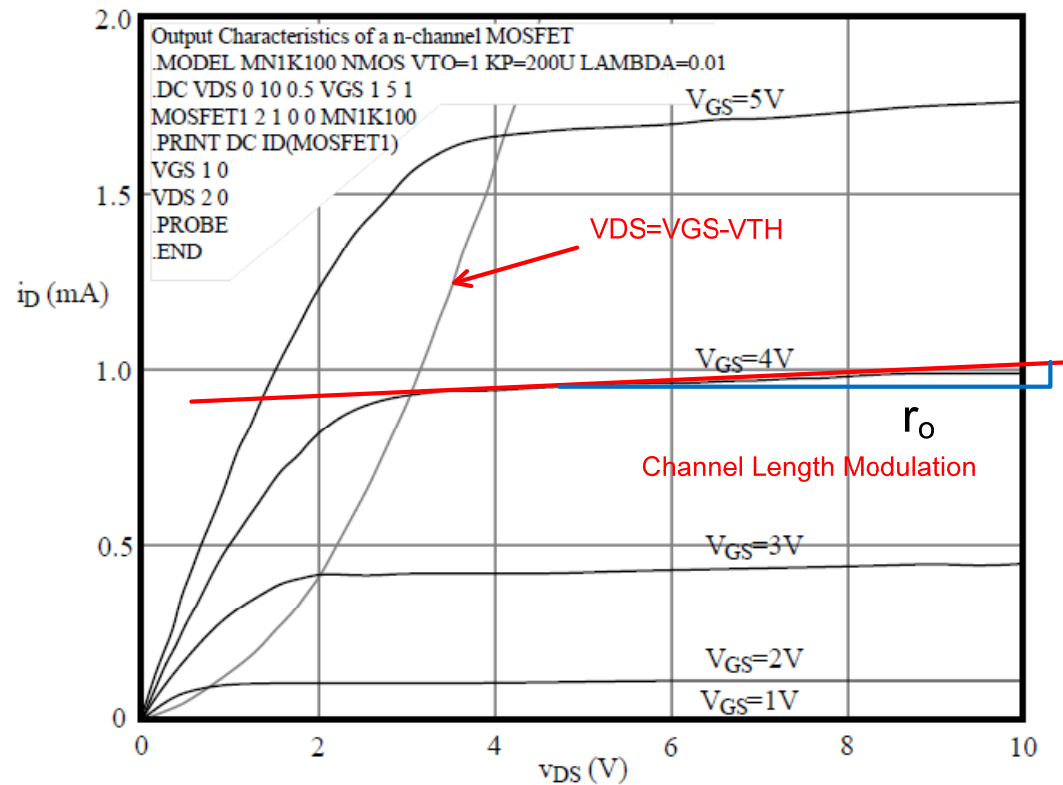


$V_{GS} = 1V$, MOS in cut-off region.

Transconductance Characteristic of NMOS:

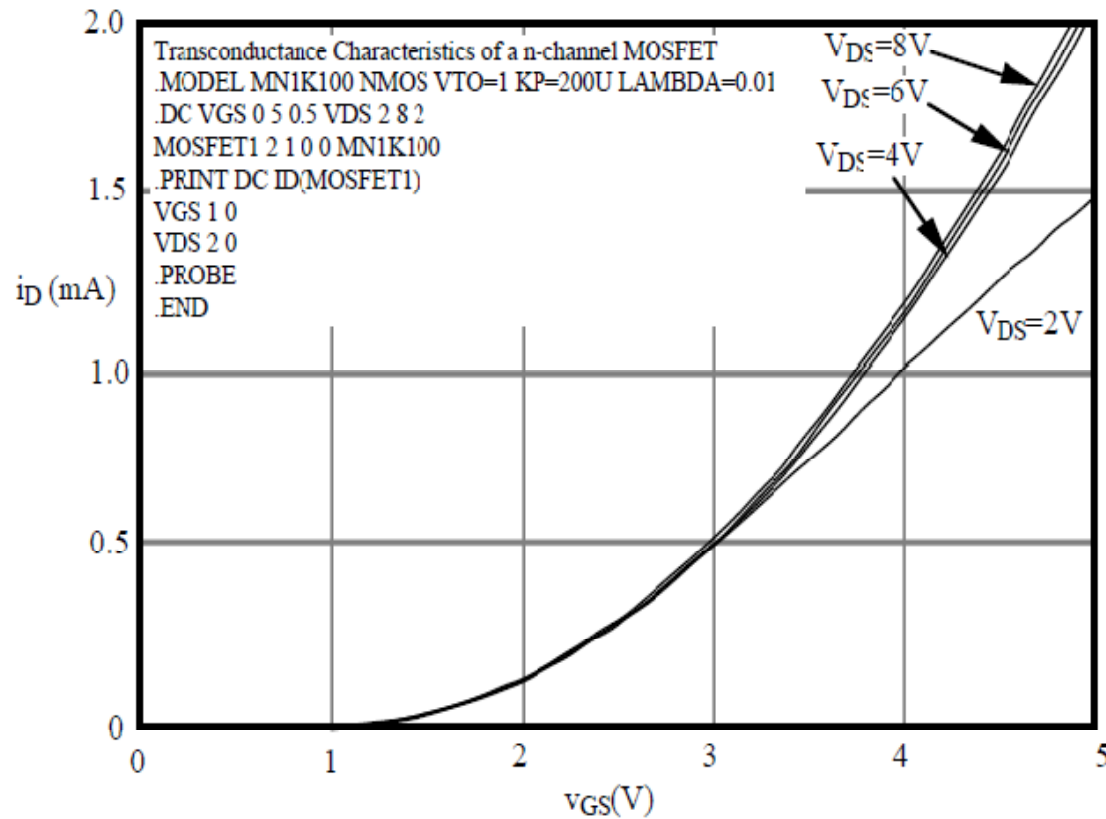

The g_m is lower at $V_{DS}=2$.

Control of Operating Region:

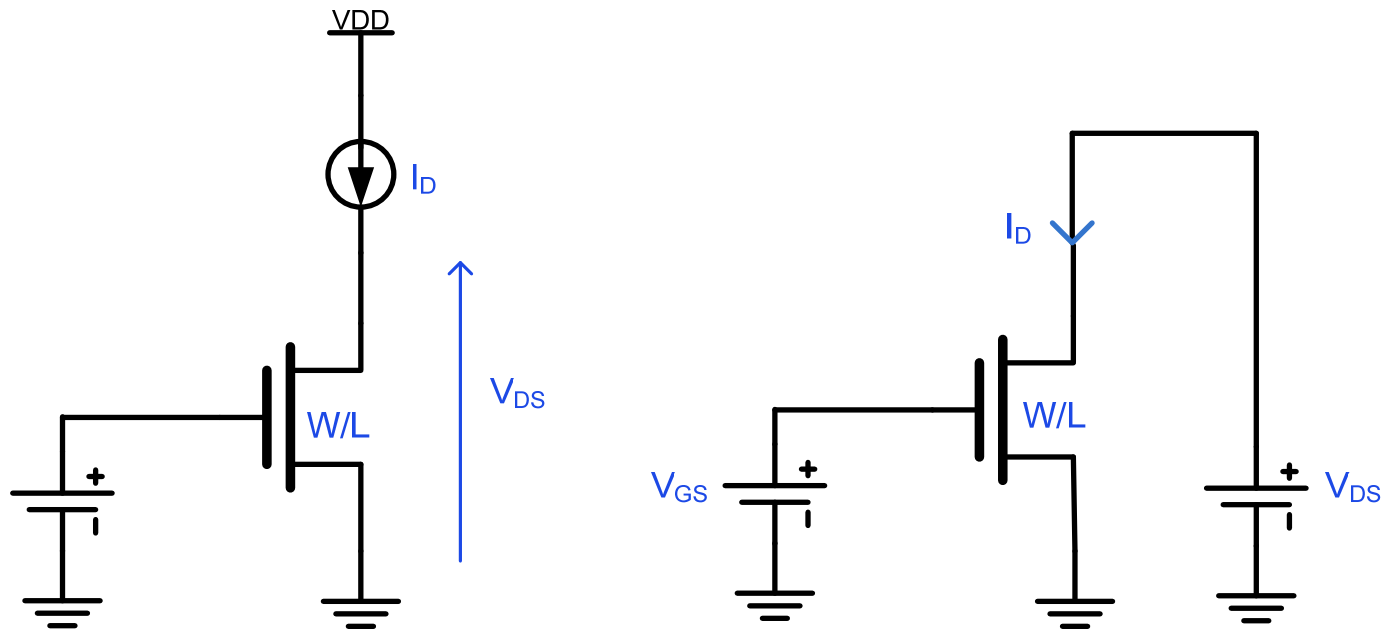

Using V_{GS} and I_D or using V_{GS} and V_{DS}




Gm:


$$\text{In active region, } I_D = \frac{1}{2} \mu_o C_{ox} \frac{W}{L} V_{OV}^2$$

$g_m = \frac{\partial I_D}{\partial V_{GS}}$	$\mu_o C_{ox} \frac{W}{L} V_{OV}$	$\sqrt{2\mu_o C_{ox} \frac{W}{L} I_D}$	$\frac{2I_D}{V_{OV}}$
$g_m \uparrow$	$\frac{W}{L} \uparrow, V_{OV} \text{ const, } I_D \uparrow$ $\frac{W}{L} \text{ const, } V_{OV} \uparrow, I_D^2 \uparrow$	$\sqrt{\frac{W}{L}} \uparrow, I_D \text{ const, } V_{OV} \downarrow$ $\frac{W}{L} \text{ const, } \sqrt{I_D} \uparrow, V_{OV} \uparrow$	$I_D \uparrow, V_{OV} \text{ const, } \frac{W}{L} \uparrow$ $I_D \text{ const, } V_{OV} \downarrow, \sqrt{\frac{W}{L}} \uparrow$
<p>Maintain V_{OV}, increase size and I_D</p> <p>Maintain size, increase overdrive and ID</p> <p>Maintain I_D, increase size and reduce overdrive → Towards sub-threshold region</p>			


Gm:

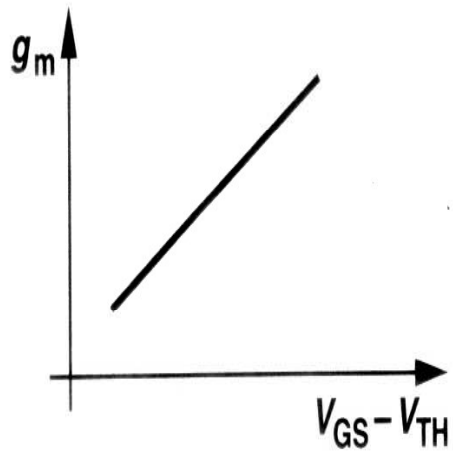

W/L Constant

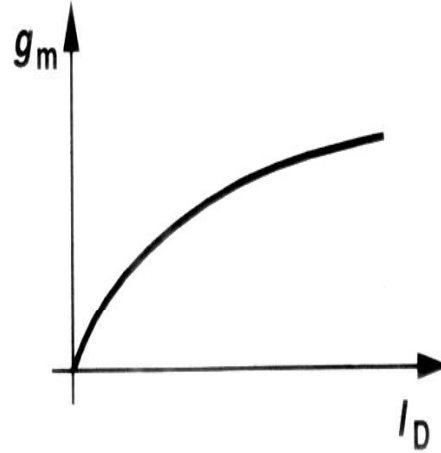


W/L Constant

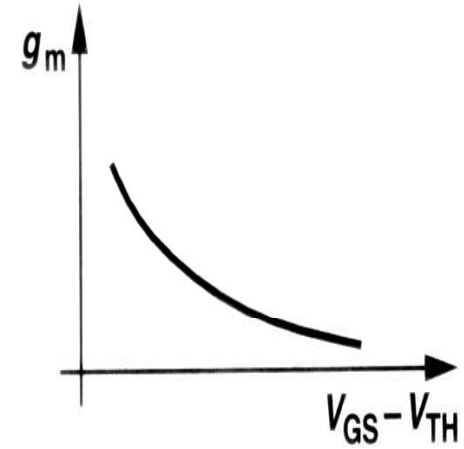

I_D Constant

Channel Length Modulation:

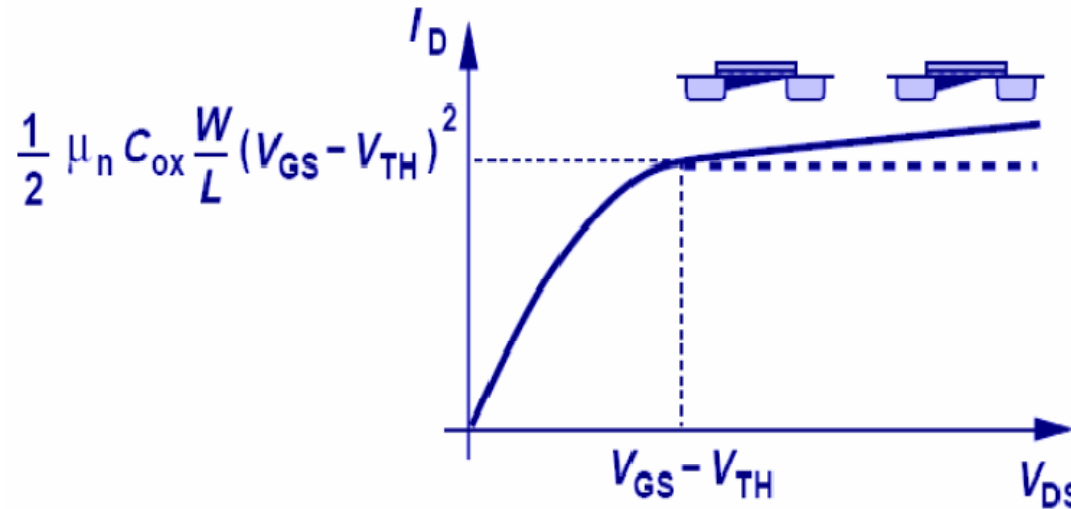

The current equation for Saturation Region is a constant since it is independent of V_{ds} . This is not true in reality. I_D in saturation region is a weak function of drain voltage.

As $V_{DS} \uparrow$, the effective channel-length, L' , decrease.



Channel Length Modulation:

$$\frac{1}{L'} = \frac{1}{L - \Delta L} = \frac{1}{L} \left(1 + \frac{\Delta L}{L} \right) = \frac{1}{L} (1 + \lambda V_{DS})$$
$$\lambda \propto \frac{1}{L}$$


λ : Channel-length modulation coefficient. It represents the relative variation in length for a given increment in VDS.

With Channel-length Modulation:

$$I_D = \frac{\mu_o C_{ox} W}{2L'} (V_{GS} - V_{TH})^2 = \frac{\mu_o C_{ox} W}{2L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$g_m = \mu_o C_{ox} \frac{W}{L} V_{OV} (1 + \lambda V_{DS}) = \sqrt{2\mu_o C_{ox} \frac{W}{L} I_D (1 + \lambda V_{DS})} = \frac{2I_D}{V_{OV}}$$

λ and L:

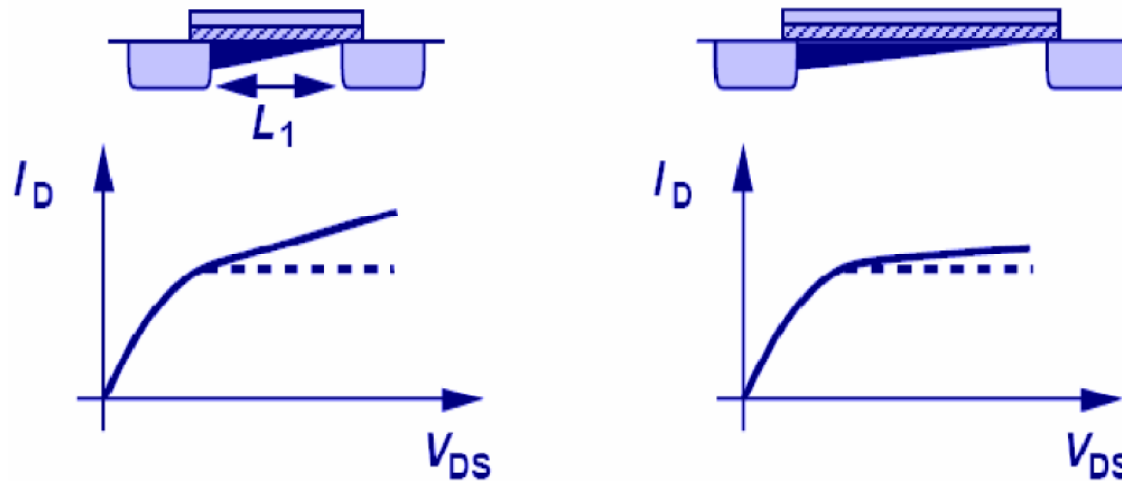


$$I_D = \frac{\mu_o C_{ox} W}{2L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$$

$$\frac{\partial I_D}{\partial V_{DS}} = \frac{\mu_o C_{ox} W}{2L} (V_{GS} - V_{TH})^2 \lambda \propto \frac{\lambda}{L} \propto \frac{1}{L^2}, \text{ since } \lambda \propto \frac{1}{L}$$

- Less channel-length modulation effect for longer L.
- If the L is doubled, the slope reduces by 4X.
- Using long L for higher ro.

Triode Region:

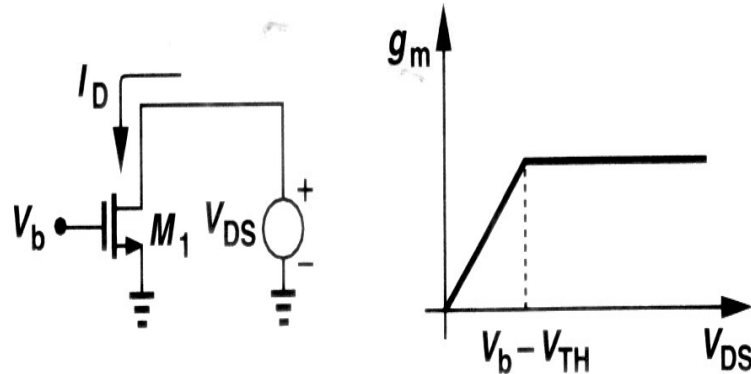


As $V_{DS} \geq V_b - V_{TH}$, M_1 is in saturation. I_D and g_m is relatively constant.

As $V_{DS} < V_b - V_{TH}$, M_1 enter triode region and:

$$g_m = \frac{\partial}{\partial V_{GS}} \left\{ \frac{\mu_o C_{ox} W}{L} \left[(V_{GS} - V_{TH}) - \left(\frac{V_{DS}}{2} \right) \right] V_{DS} \right\} = \mu_o C_{ox} \frac{W}{L} V_{DS}$$

In triode region, as $V_{DS} \downarrow$, $g_m \downarrow$. No gain in triode region.

Triode Region: R_{ON}

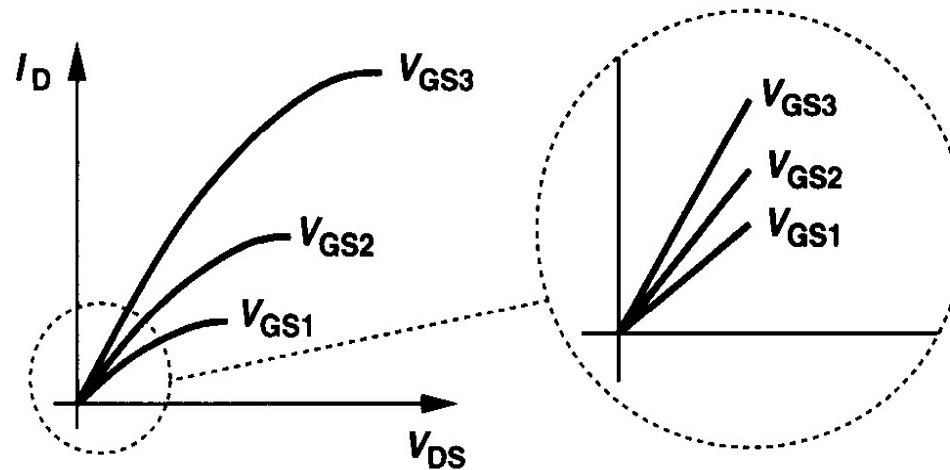




In triode region, if $V_{DS} \ll V_{GS} - V_{TH}$

$$I_D = \frac{\mu_o C_{ox} W}{L} \left[(V_{GS} - V_{TH}) - \left(\frac{V_{DS}}{2} \right) \right] V_{DS} \approx \mu_o C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) V_{DS}$$

$$R_{ON} = \frac{1}{\mu_o C_{ox} \frac{W}{L} (V_{GS} - V_{TH})}$$

To reduce R_{ON} , increase the size or increase the overdrive voltage.

Effect of Back Gate:

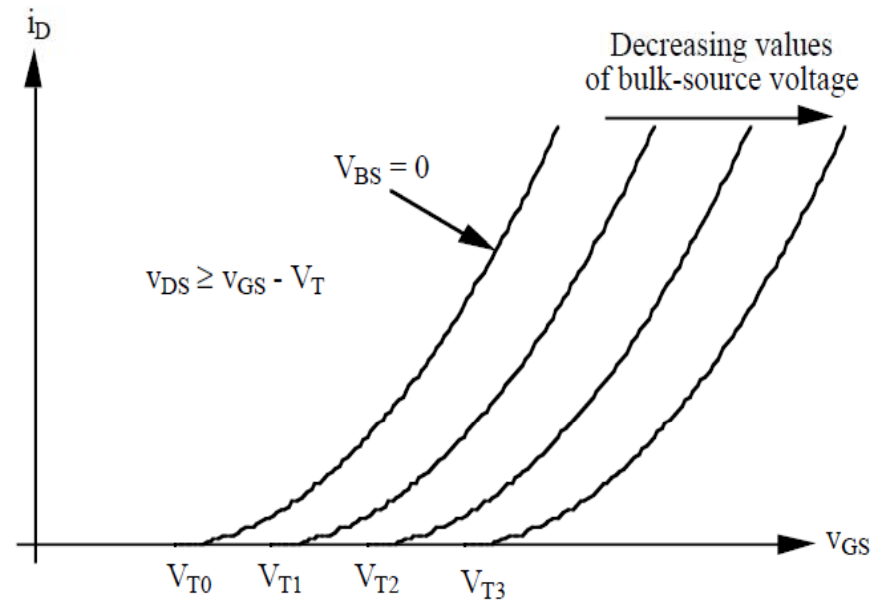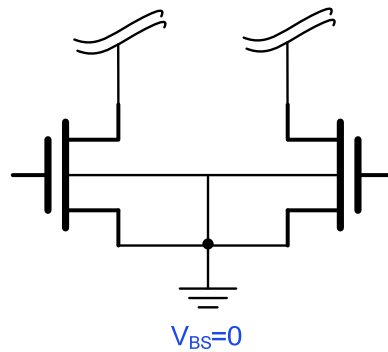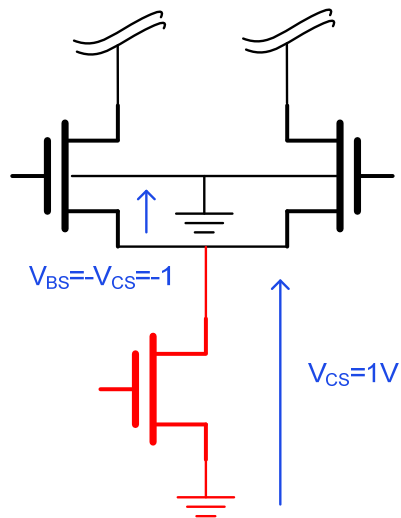

With $V_{BS} < 0$, more difficult to turn on the NMOS.

With $V_{BS} > 0$, easier to turn on the NMOS.



Threshold Voltage, V_{TH} :

Zero bias ($V_{BS}=0$) threshold voltage: $V_{TH0} = \Phi_{MS} + 2\Phi_F + \frac{Q_{dep}}{C_{ox}}$

Φ_{MS} = difference between work functions of the polysilicon gate and the silicon substrate

Φ_F = strong inversion surface potential (V)


Q_{dep} = charge in depletion region

Threshold voltage:


$$V_{TH} = V_{TH0} + \gamma \left(\sqrt{|2\Phi_F + V_{SB}|} - \sqrt{|2\Phi_F|} \right)$$

γ = body effect coefficient


Small Signal Model:

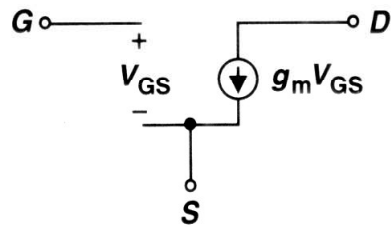


(a)

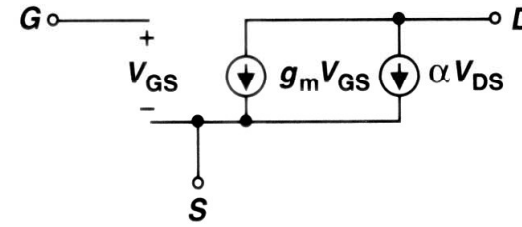

(b)

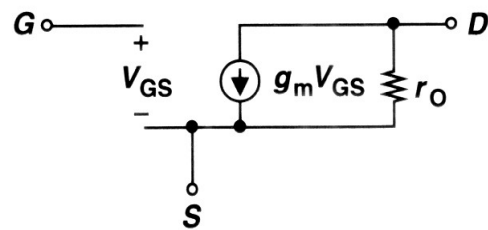

(c)

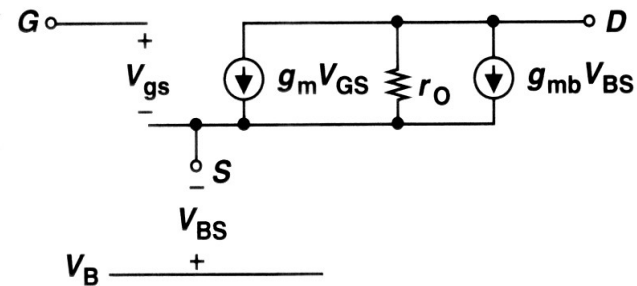

(d)



Small Signal Model:

An approximation of the large-signal model around the operating point (DC-bias).

Channel length modulation $\rightarrow I_D$ varies with $V_{DS} \rightarrow$ Resistor.

$$r_o = \frac{1}{\partial I_D / \partial V_{DS}} = \frac{1}{\frac{\mu_o C_{ox} W}{2L} (V_{GS} - V_{TH})^2 \lambda} \approx \frac{1}{\lambda I_D}$$

R_o , the output impedance will limit the voltage gain of amplifier.

$G_m \cdot r_o$ is called **intrinsic gain** of the transistor.

Bulk potential affects threshold voltage and hence the GS overdrive voltage.

$$g_{mb} = \frac{\partial I_D}{\partial V_{BS}} = \mu_o C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \left(-\frac{\partial V_{TH}}{\partial V_{BS}} \right) = g_m \frac{\gamma}{2\sqrt{2\Phi_F + V_{SB}}} = \eta g_m$$

$g_m V_{GS}$ and $g_{mb} V_{SB}$ have the same polarity.

Raising the gate voltage has the same effect as raising the bulk potential.

Complete MOS Small-signal Model:

