

1. **RF Amplifier Design**

This report describes the design of a RF amplifier operating at 2.4GHz.

Below are the design specifications: -

Centre Frequency	2.4 GHz
Bandwidth	$\pm 5\%$
Noise Figure	<3dB
Gain	As high as possible
Source impedance	$50\ \Omega$
Load impedance	$50\ \Omega$
Size of Circuit Layout	4" x 5"

The transistor used here is Fujitsu FHX35LG HEMT.

2. Design Procedure

The available power gain approach, where the output is assumed conjugate match, is used here.

a. Transistor performance

Firstly the performance of the FHX35LG transistor is evaluated.

Base on the S-parameter of the transistor at 2.4 GHz (Fig 2).


$$\begin{aligned}\Delta &= S_{11}S_{22}-S_{12}S_{21} \\ &= 0.464 \angle -71.7^\circ \\ |\Delta| &= 0.464 < 1\end{aligned}$$

$$\begin{aligned}K &= (1+|\Delta|^2-|S_{11}|^2-|S_{22}|^2) / (2*|S_{12}S_{21}|) \\ &= 0.239 < 1\end{aligned}$$

Therefore the transistor is conditionally stable at 2.4GHz. It is also found that the transistor is conditional stable up to 12GHz as shown in Fig 1.

This will present difficulty in the amplifier design, as the microstrip matching network designed for 2.4GHz may not ensure stability at other frequencies thus resulting oscillations.

Figure 1 FHX35LG Stability Gain and Noise Plot @ 2.4GHz


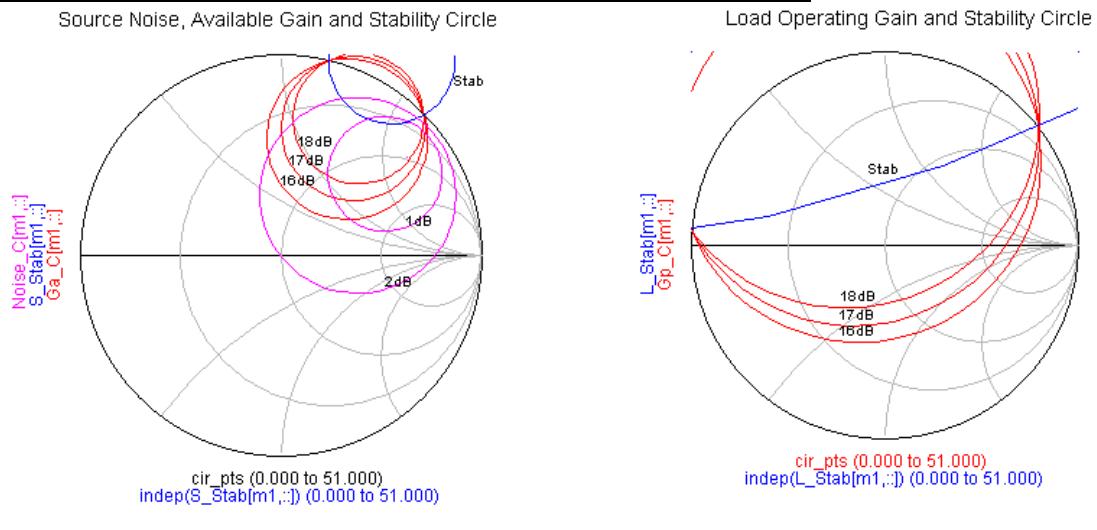


freq	K	Δ	Delta
1.900GHz	0.204		0.480
2.000GHz	0.209		0.477
2.100GHz	0.217		0.474
2.200GHz	0.225		0.471
2.300GHz	0.232		0.467
2.400GHz	0.239		0.464
2.500GHz	0.246		0.460
2.600GHz	0.252		0.457
2.700GHz	0.258		0.453
2.800GHz	0.264		0.450
2.900GHz	0.270		0.446


Figure 2 Transistor S Parameter @ 2.4GHz

S(1,1)[m1]	S(1,2)[m1]	S(2,1)[m1]	S(2,2)[m1]
0.935 / -52.660	0.049 / 52.580	4.193 / 131.980	0.492 / -44.760


Therefore it is necessary to stabilize the transistor using external component. Firstly, output series resistor of 30 ohm will be used to stabilize the high frequency performance. Secondly, to reduce the Q of the matching network a microstrip line is used to shift the gain and stability circles closer to the real axis. Thirdly, a 36-ohm shunt resistor at the input will be used to stabilize the low frequency performance.

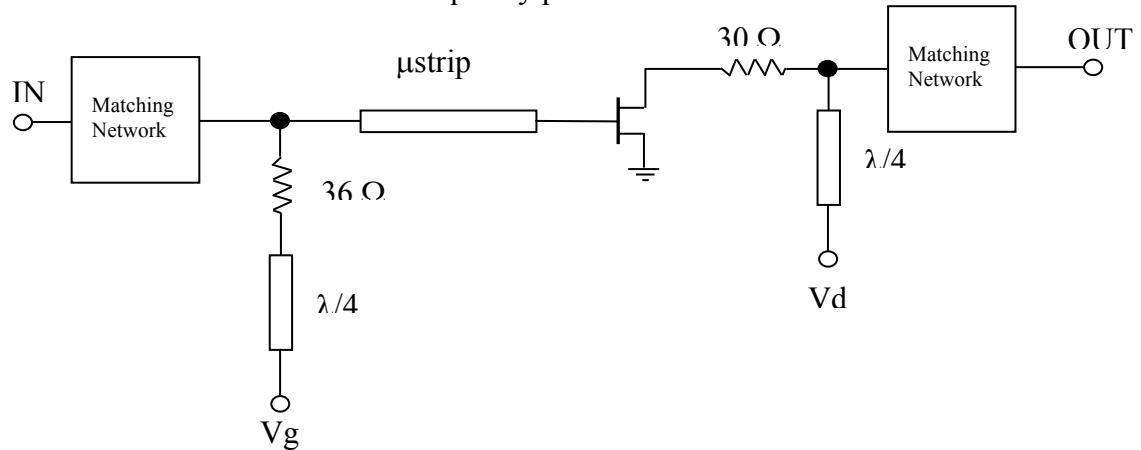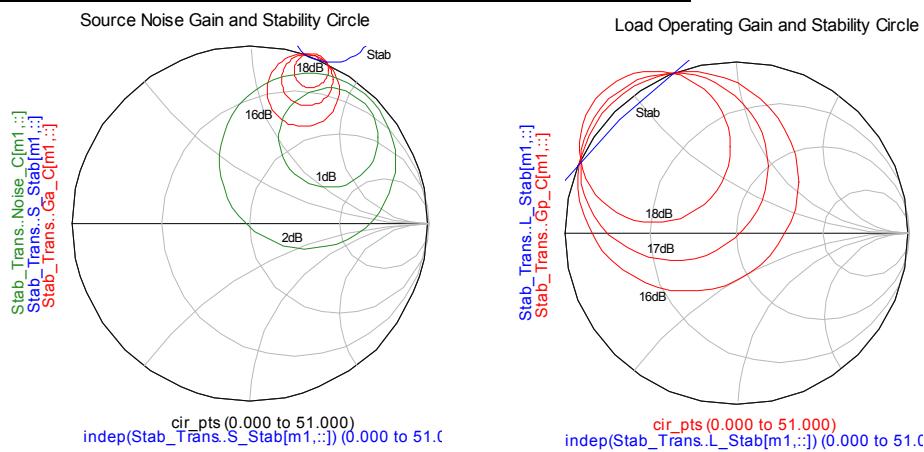**Figure 3 Performance with output series resistance**

Observation : Gain circle radius reduced and K value improved for higher frequencies.

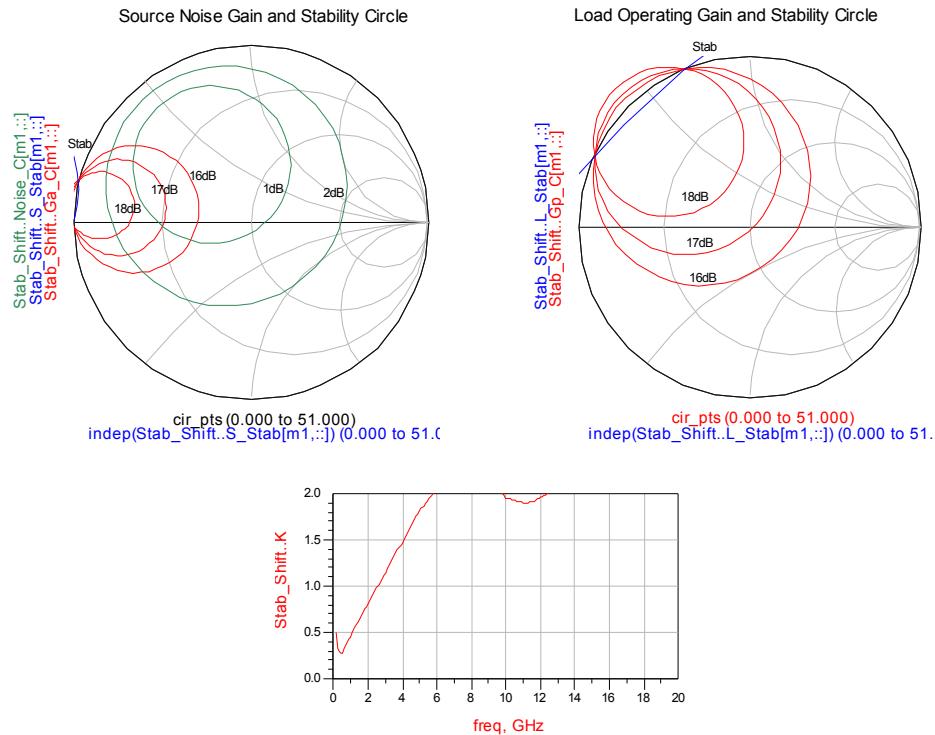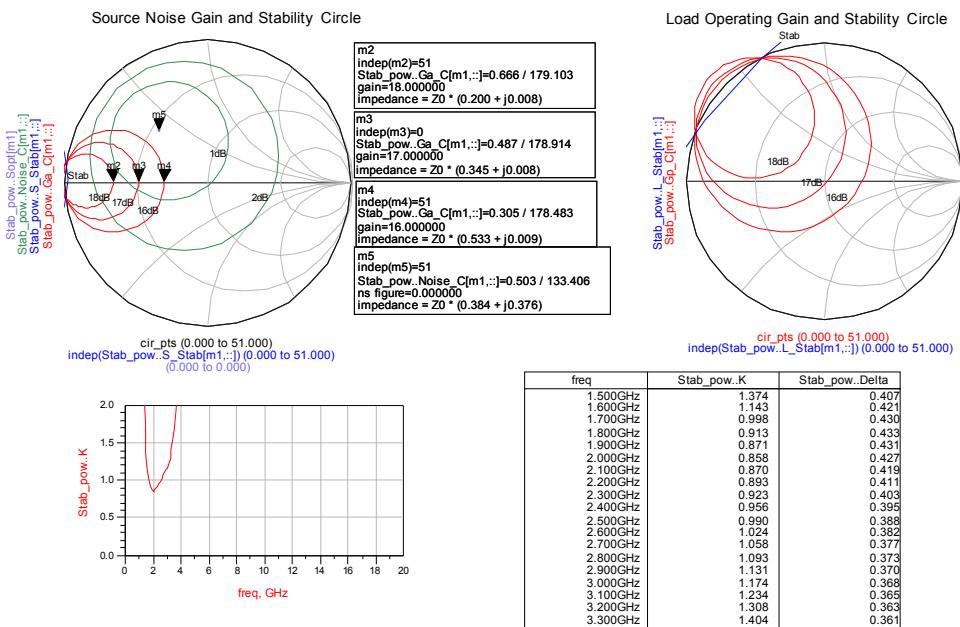Figure 4 Performance with 330 mils micro strip

Observation : Both noise and gain circles shift closer to the real axis.

Figure 5 Performance with input shunt resistor 36 ohm

Observation: K value improved for the lower frequencies.

Figure 6 S-parameter of final stabilized circuit

Stab_pow..S(1,1)[m1]	Stab_pow..S(1,2)[m1]	Stab_pow..S(2,1)[m1]	Stab_pow..S(2,2)[m1]
0.729 / -171.699	0.056 / -32.734	4.881 / 41.870	0.317 / -76.703

$$\begin{aligned}
 \Delta &= S_{11}S_{22}-S_{12}S_{21} \\
 &= 0.394\angle 154.2^\circ \\
 |\Delta| &= 0.394 < 1 \\
 K &= (1+|\Delta|^2-|S_{11}|^2-|S_{22}|^2) / (2*S_{12}S_{21}) \\
 &= 0.957 < 1
 \end{aligned}$$

Input stability Circle :

$$\begin{aligned}
 r_s &= |S_{12}S_{21}| / (|S_{11}|^2-|\Delta|^2) \\
 &= 0.726 \\
 C_s &= (S_{11}^*-\Delta^*S_{22}) / (|S_{11}|^2-|\Delta|^2) \\
 &= 1.708\angle 179.25^\circ
 \end{aligned}$$

Output stability Circle :

$$\begin{aligned}
 r_L &= |S_{12}S_{21}| / (|S_{22}|^2-|\Delta|^2) \\
 &= 4.99 \\
 C_L &= (S_{22}^*-\Delta^*S_{11}) / (|S_{22}|^2-|\Delta|^2) \\
 &= 4.04\angle -41.8^\circ
 \end{aligned}$$

Noise Circle @ 1dB :

$$\begin{aligned}
 N_i &= (F_i - F_{min}) * |1 + \Gamma_o|^2 / 4r_n \\
 &= (1.26 - 1.139) * |1 + 0.503\angle 133.4^\circ|^2 / (4 * 0.063) \\
 &= 0.270 \\
 C_{Fi} &= \Gamma_o / (1 + N_i) \\
 &= 0.396\angle 133.4^\circ \\
 r_{Fi} &= \sqrt{(N_i^2 + N_i(1 - |\Gamma_o|^2)) / (1 + N_i)} \\
 &= 0.4126
 \end{aligned}$$

From Fig 5, Γ_s of $0.487\angle 179^\circ$ is chosen.

$$\begin{aligned}
 \Gamma_{out} &= (S_{22} - \Delta\Gamma_s) / (1 - S_{11}\Gamma_s) \\
 &= 0.3738\angle -109.9^\circ \implies \text{Located within the load stable region}
 \end{aligned}$$


Therefore Γ_s of $0.487\angle 179^\circ$ is OK.

b. Input Matching Network

Two step approach is used here. Initial design is done using smithchart than the values are tuned using ADS. A balanced double stud is used here.

Fig 7 shows the input matching network adopted and Page 7 shows the smith chart matching calculation and working.

Figure 7 Simplified Input Matching Network

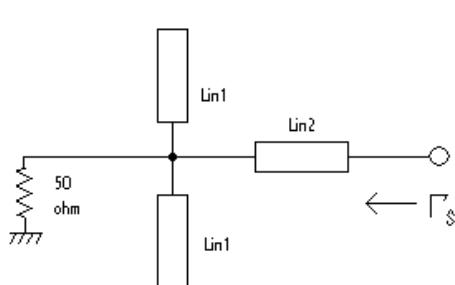

The calculated value are
Lin1=287 mils
Lin2=302 mils

This value are fine tuned using ADS to give
Lin1=260 mils
Lin2=285 mils


Schematic and results are shown in page 8 & 9.

$$\lambda = \frac{c}{\sqrt{\epsilon_{eff}}}$$

$\lambda = 3510$ mils (from Line Calc)

$$l_{in1} = 287 \text{ mils}$$

$$l_{in2} = 302.25 \text{ mils}$$

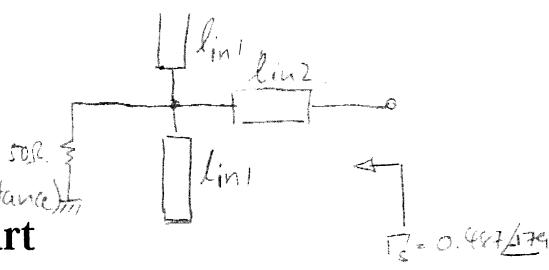

The Complete Smith Chart

Black Magic Design

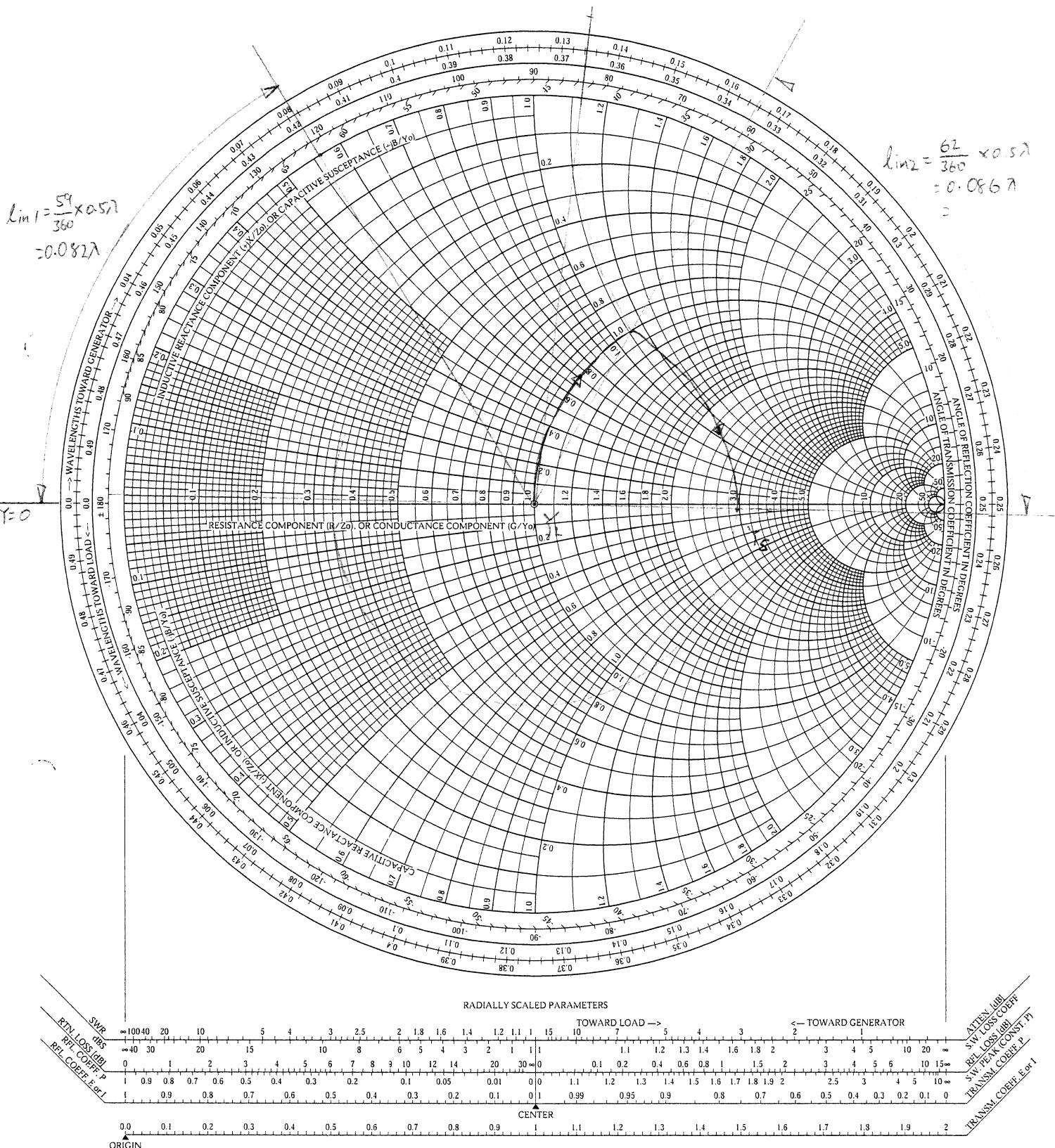


Figure 8 Input Matching Network


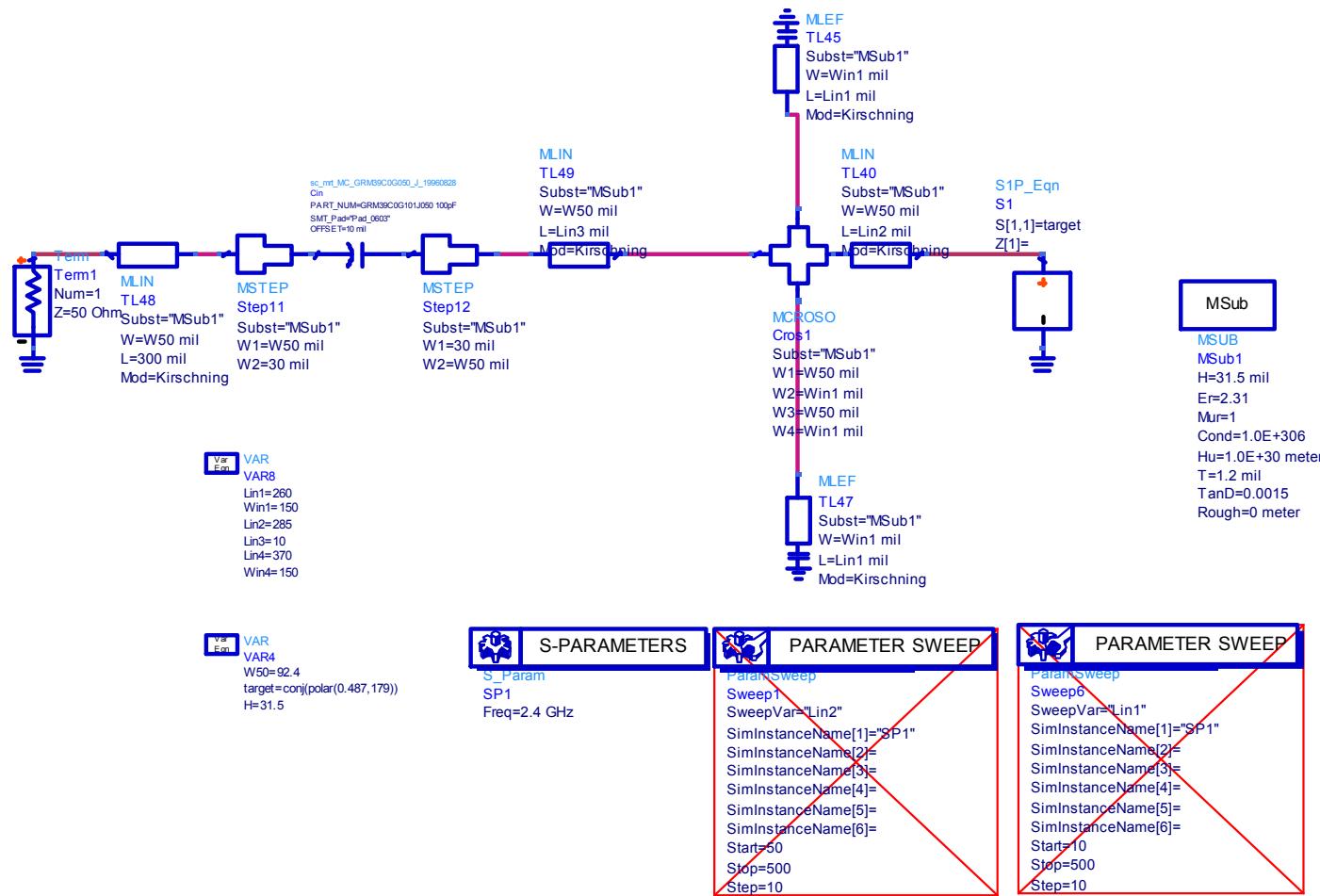


Figure 9 Input Matching Smith Chart

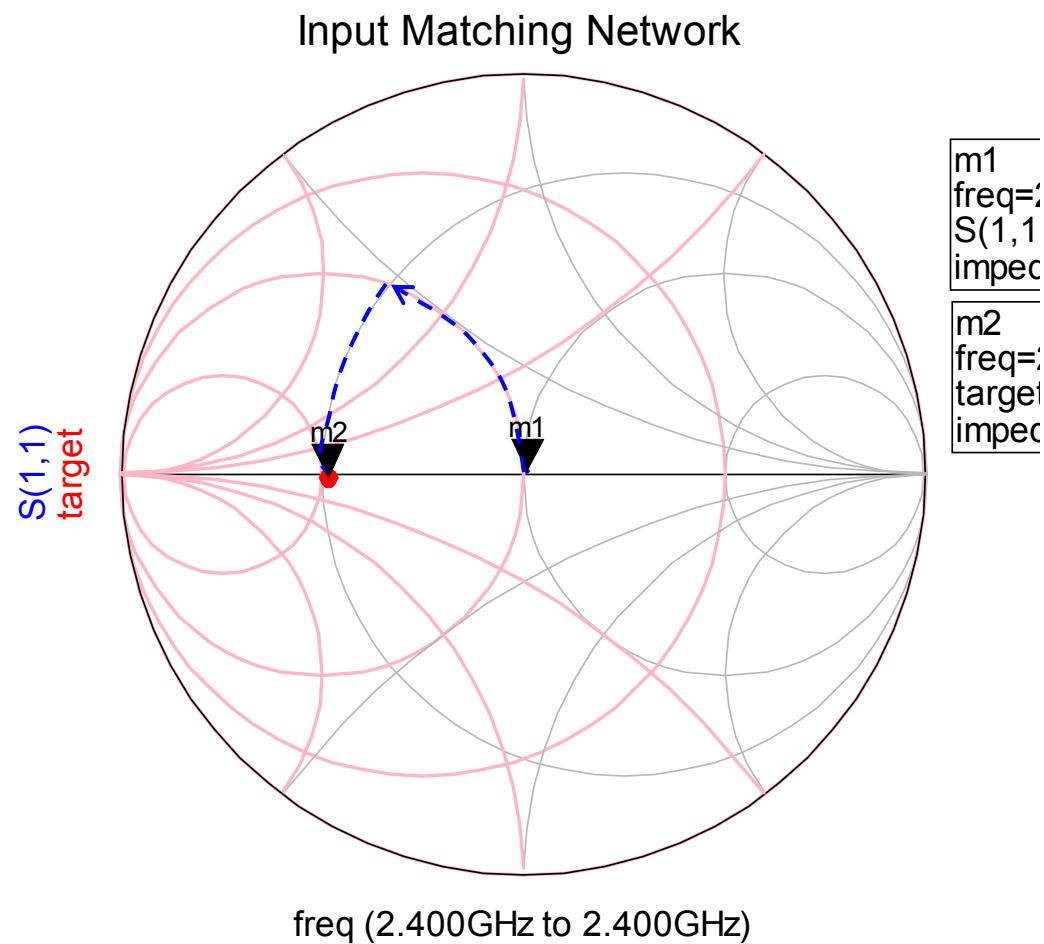


c. Output Matching Network

The designed input matching network is combined with the stabilized transistor network to simulate the resulting Γ_{out} . (Pg 11 & 12)

$$\Gamma_{out} = 0.384 \angle -110^\circ \quad (\text{Calculated } \Gamma_{out} = 0.3738 \angle -109.9^\circ)$$

Fig 10 shows the output-matching network adopted and Page 13 shows the smith chart matching calculation and working.


Figure 10 Simplified Output Matching Network

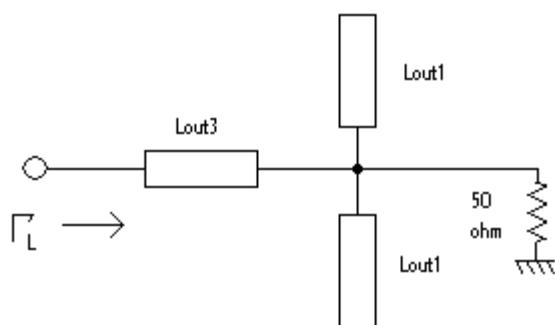


The calculated value are $L_{out1}=224$ mils
 $L_{out3}=667$ mils

This value are fine tuned using ADS to give
 $L_{out3}=195$ mils
 $L_{out3}=660$ mils

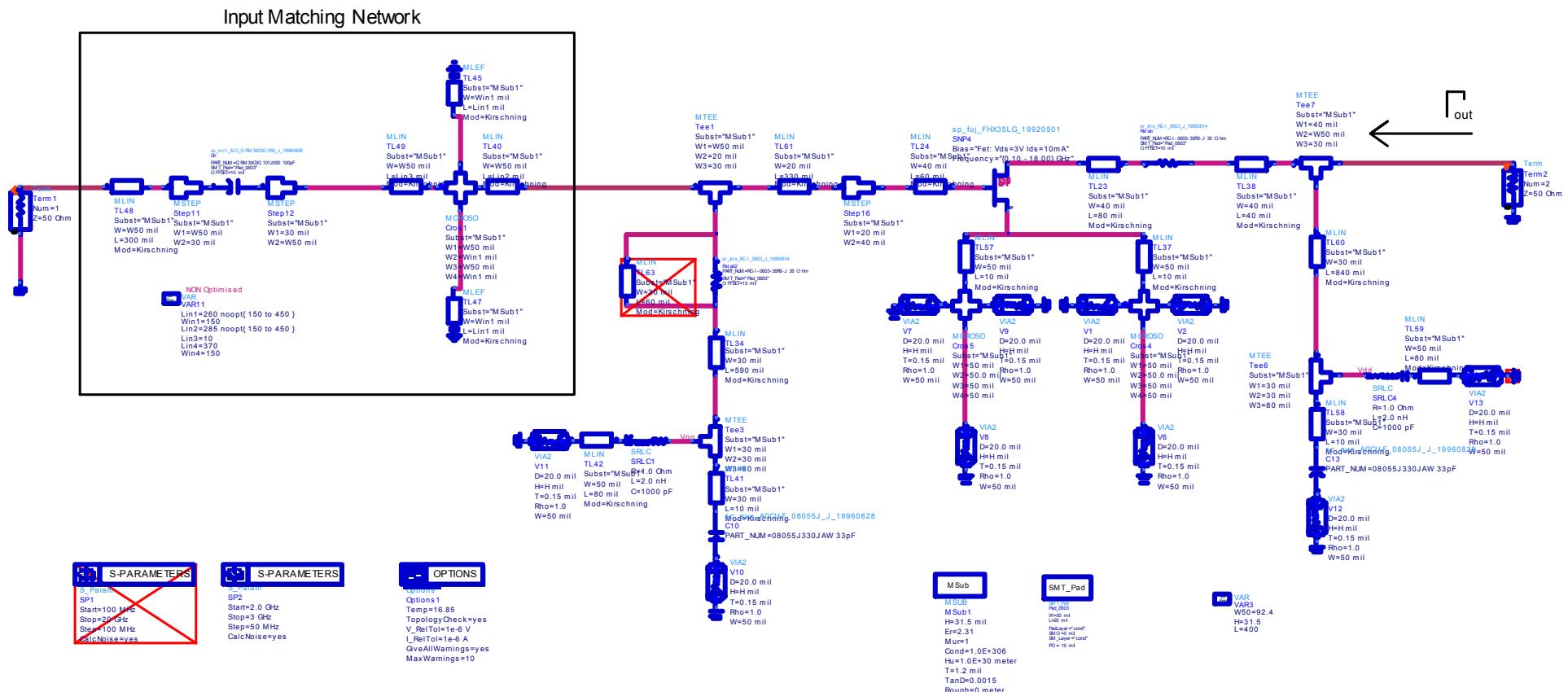Schematic and results are shown in page 14 & 15.




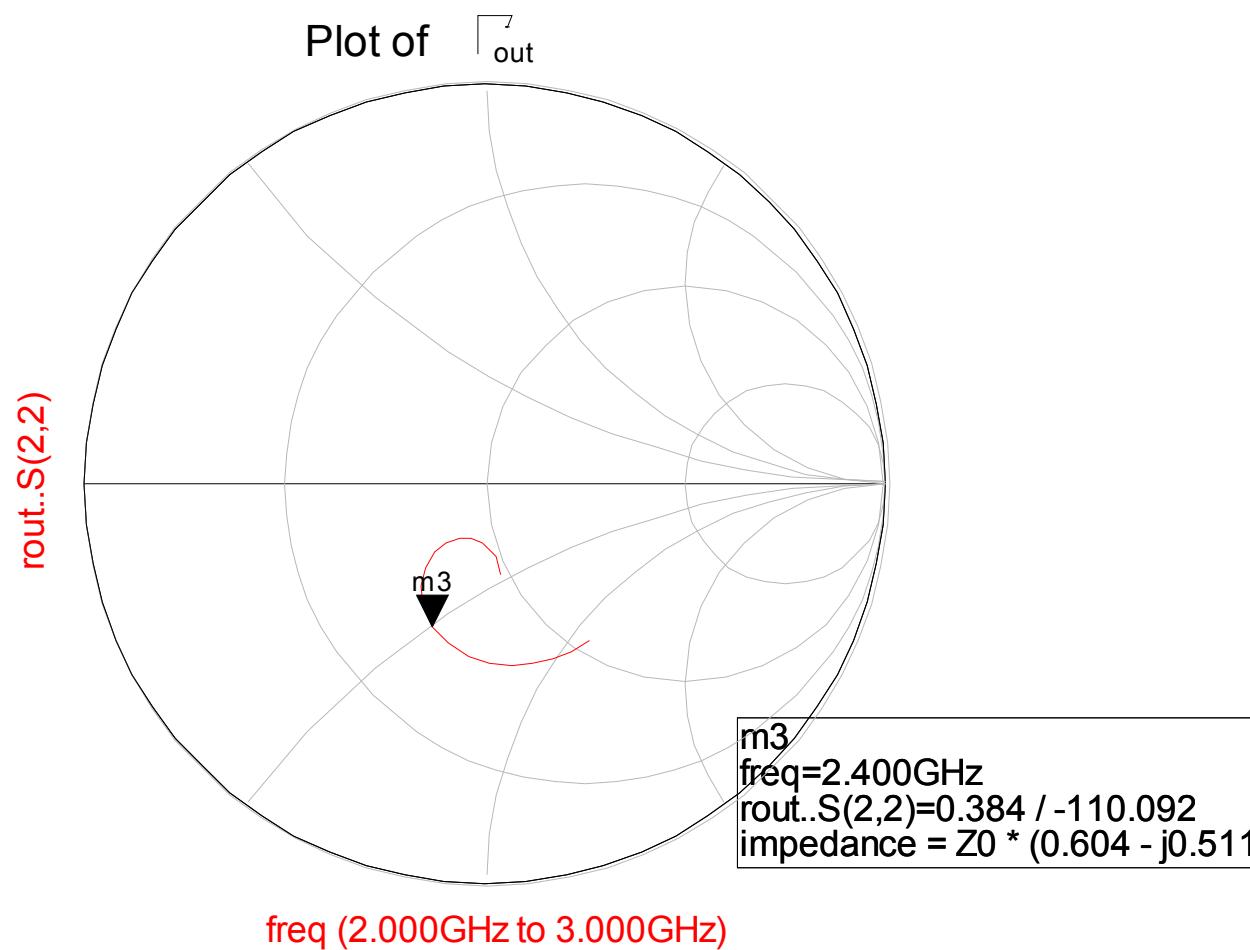

$$\lambda = 3510$$

lout1 = 224 mils

$$l_{out3} = 667.9 \text{ mils}$$

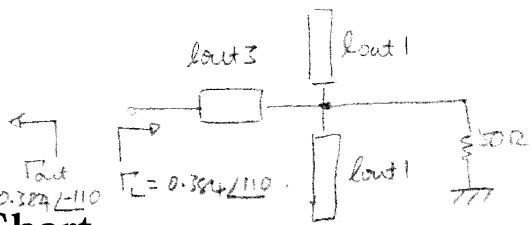

Output Matching Network Fat 0.324 L/10

The Complete Smith Chart



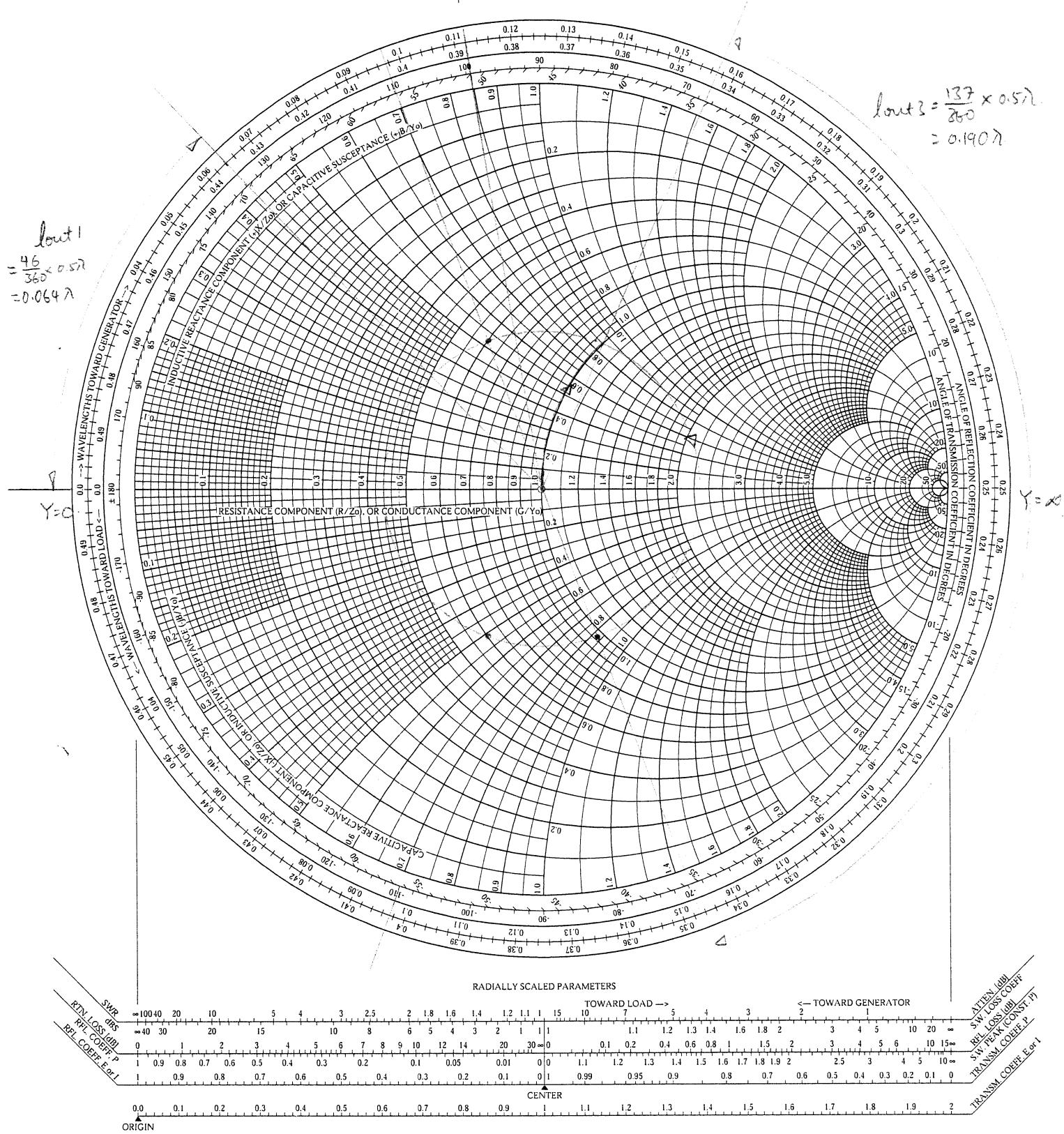


Figure 11 Output Matching Network

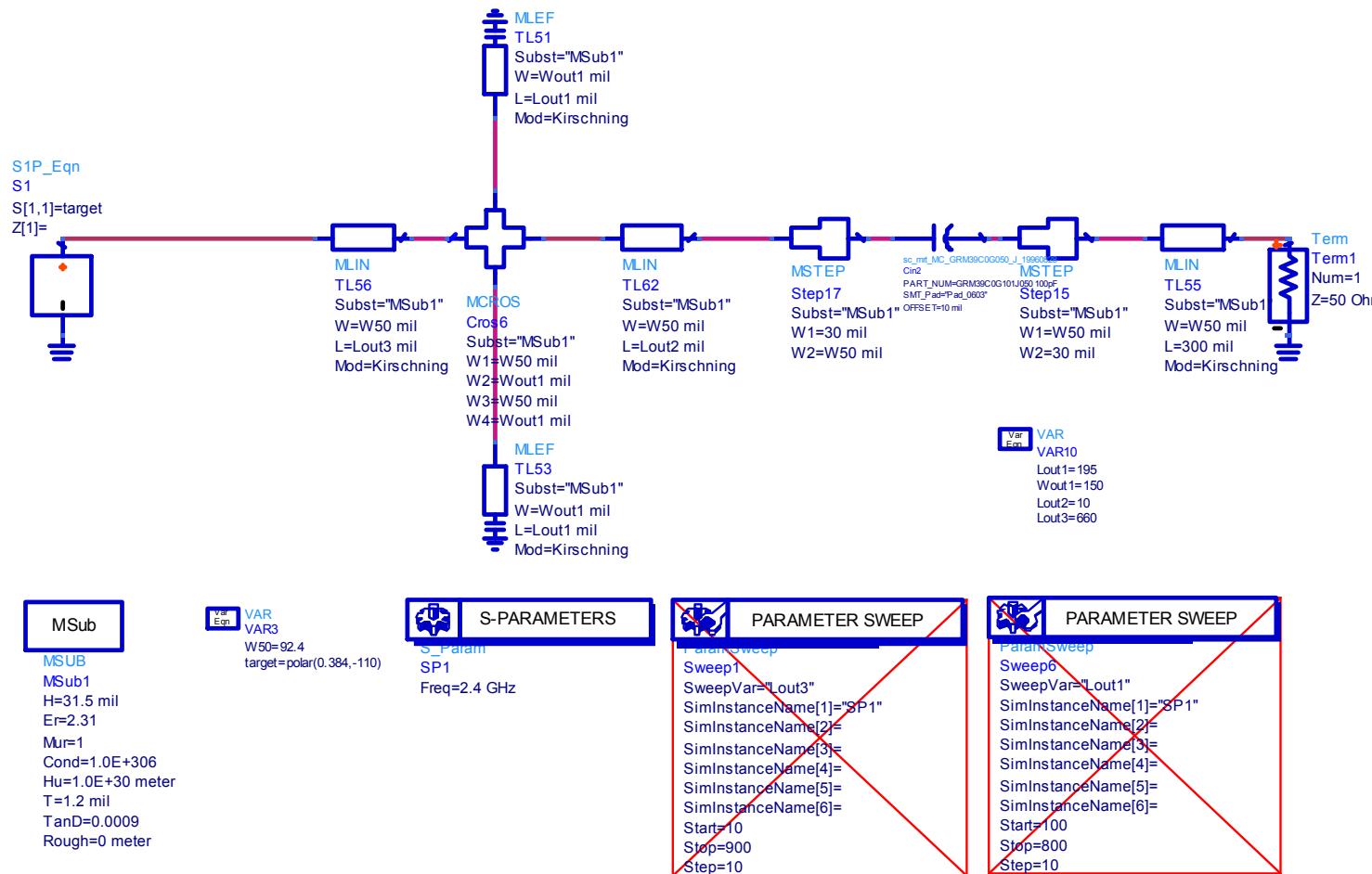

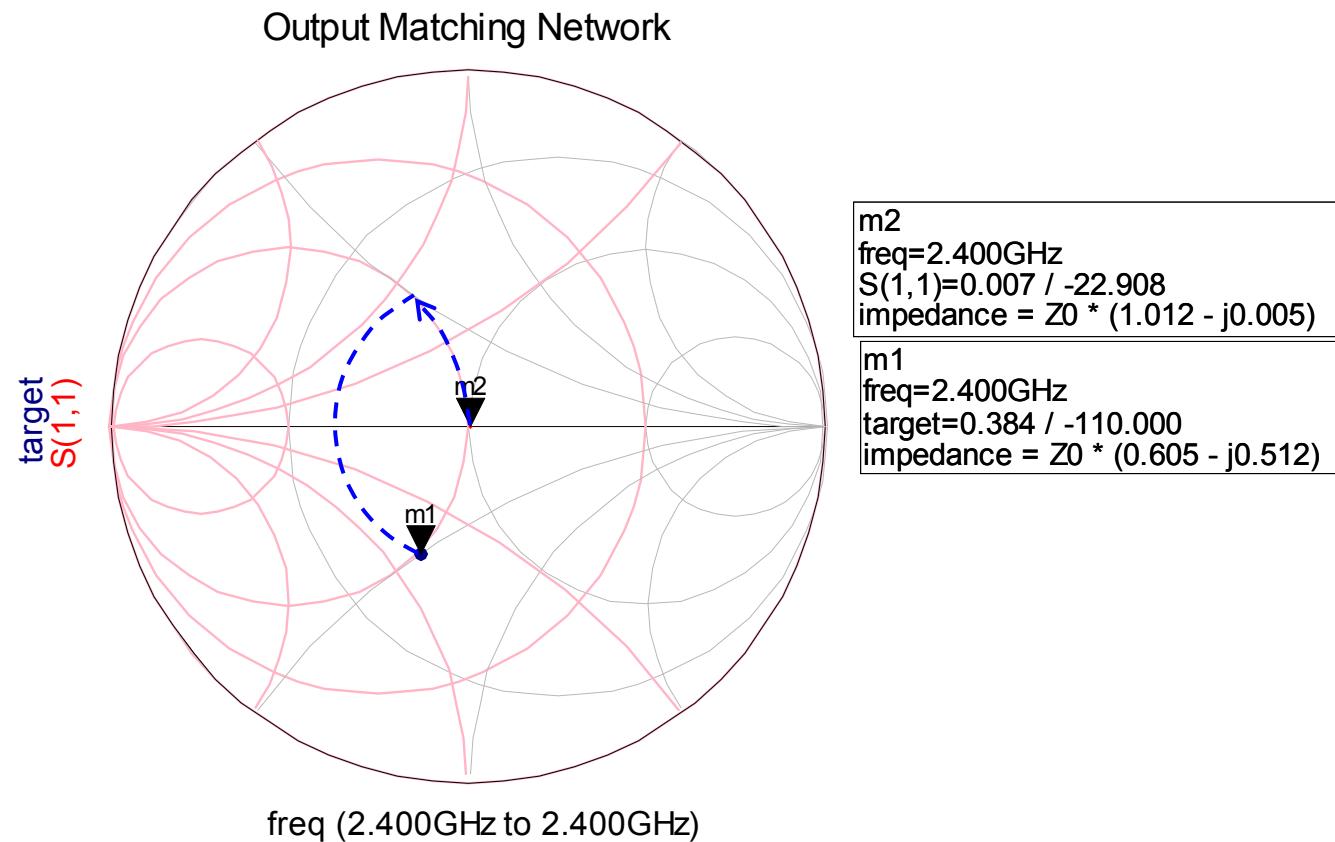

d. Final Amplifier Schematic


The designed input and output-matching network are finally combined together with the transistor and simulated.


Page 18 shows the performance of the amplifier using the parameters before optimization.


Page 19 shows the performances after optimization.


Final optimized matching network parameters are

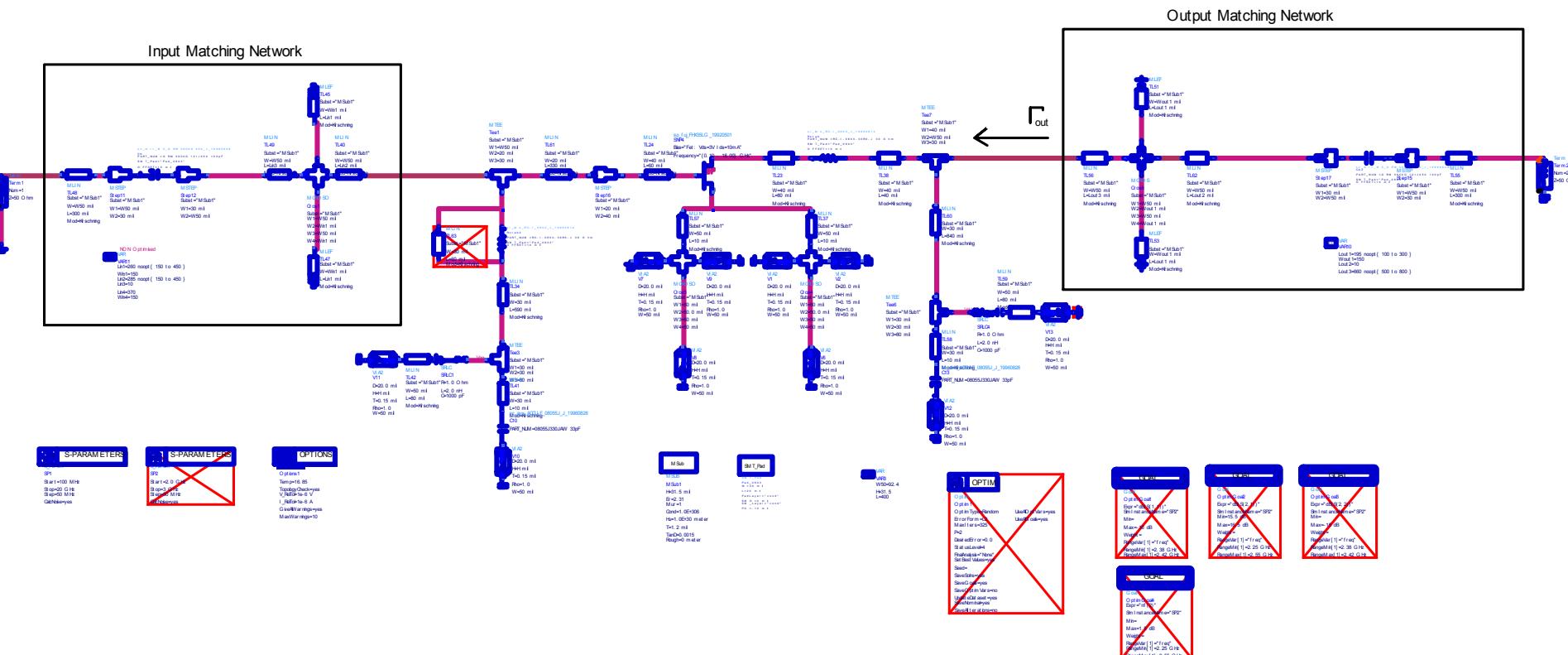Lin1 = 313 mils Lin2 = 212 mils
Lout3 = 204 mils Lout3 = 738 mils



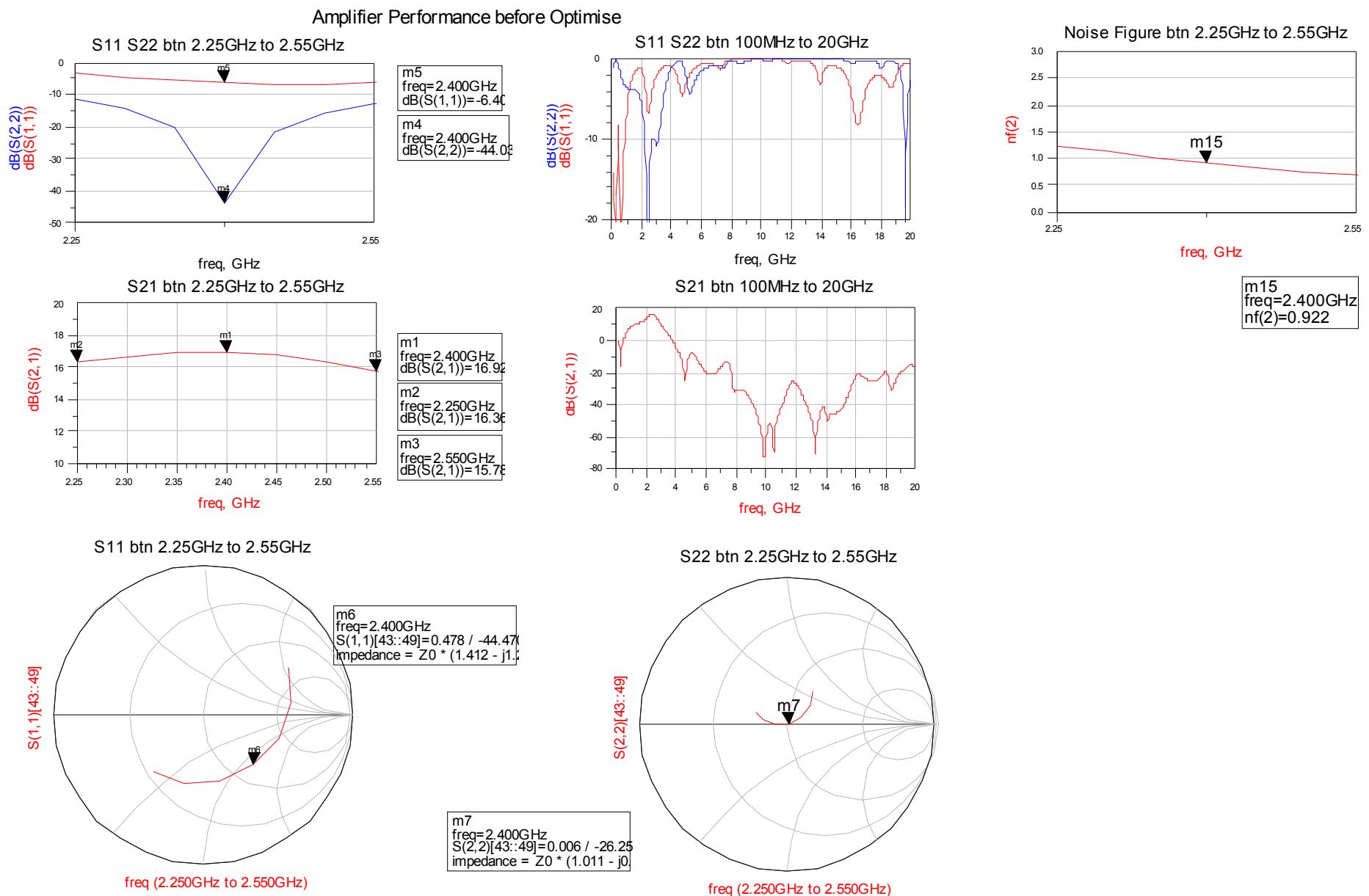

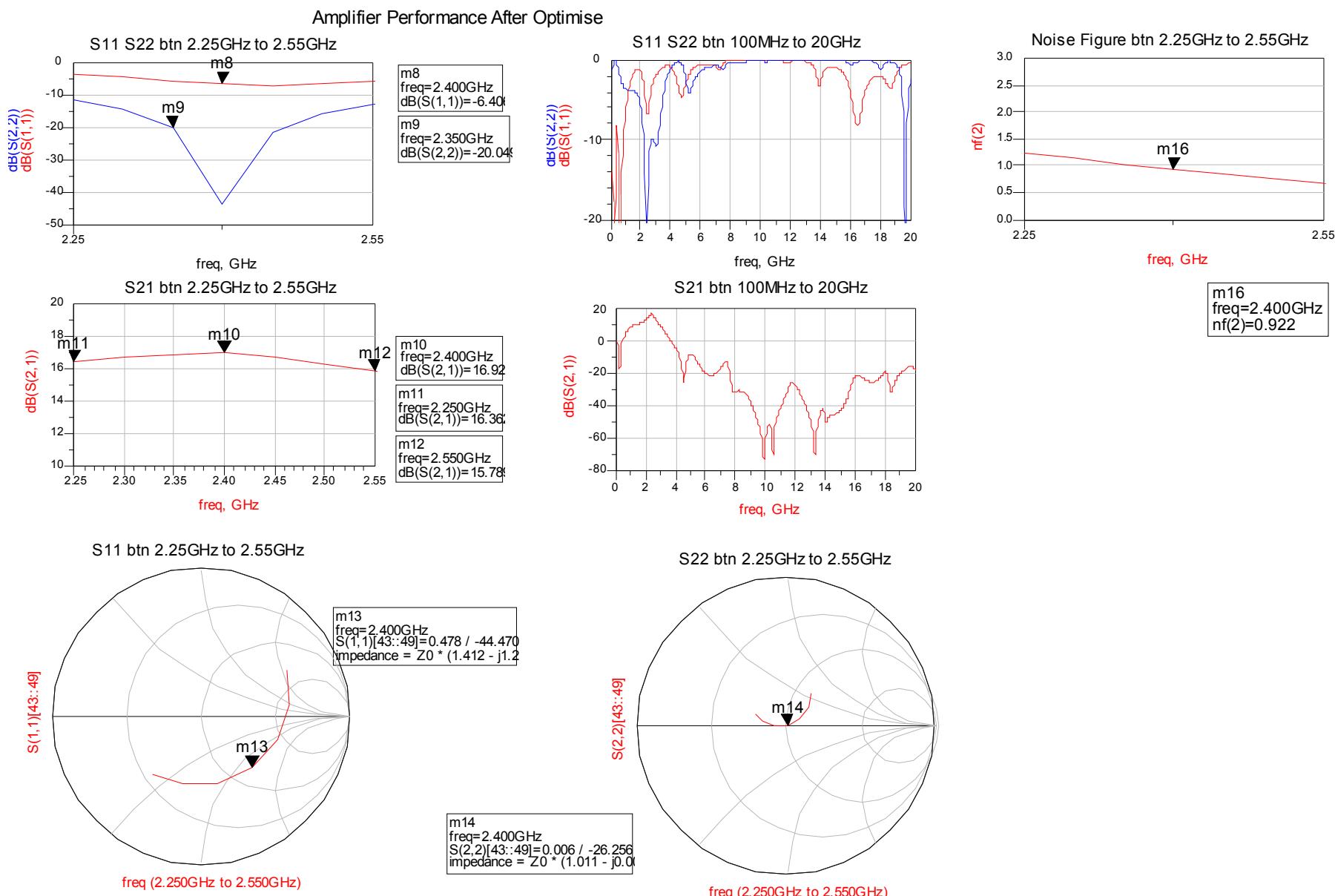

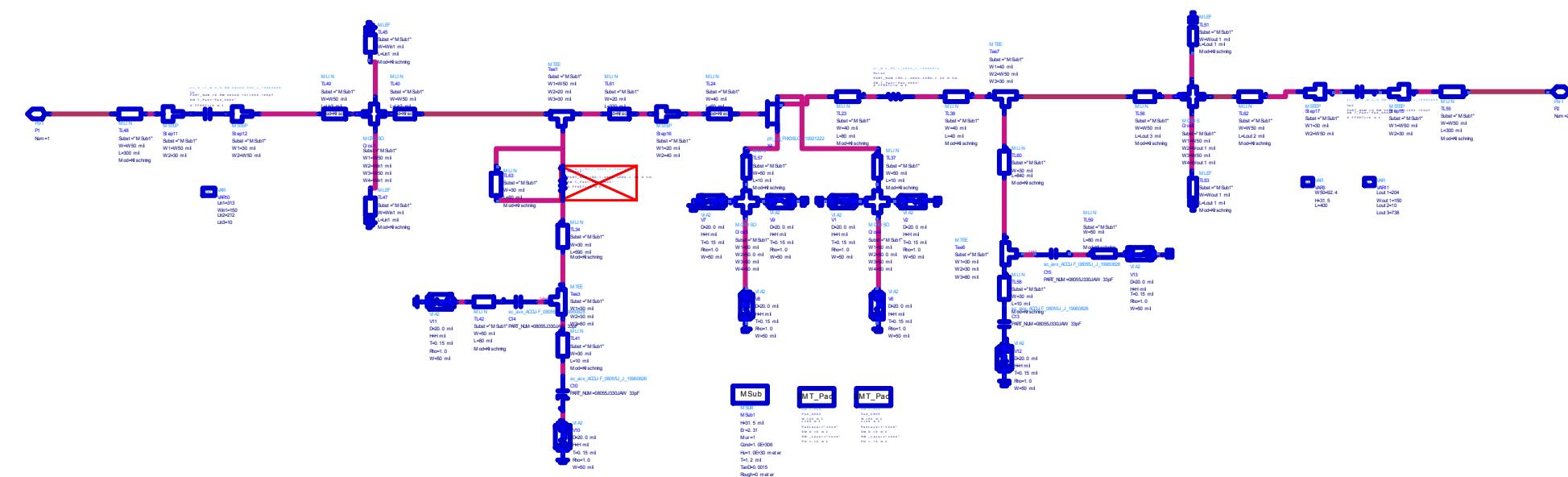

Note : Final schematic and layout will exclude the input stabilizing resistor (36 ohm) for the time being. If low frequency oscillation is observed, it will be added.

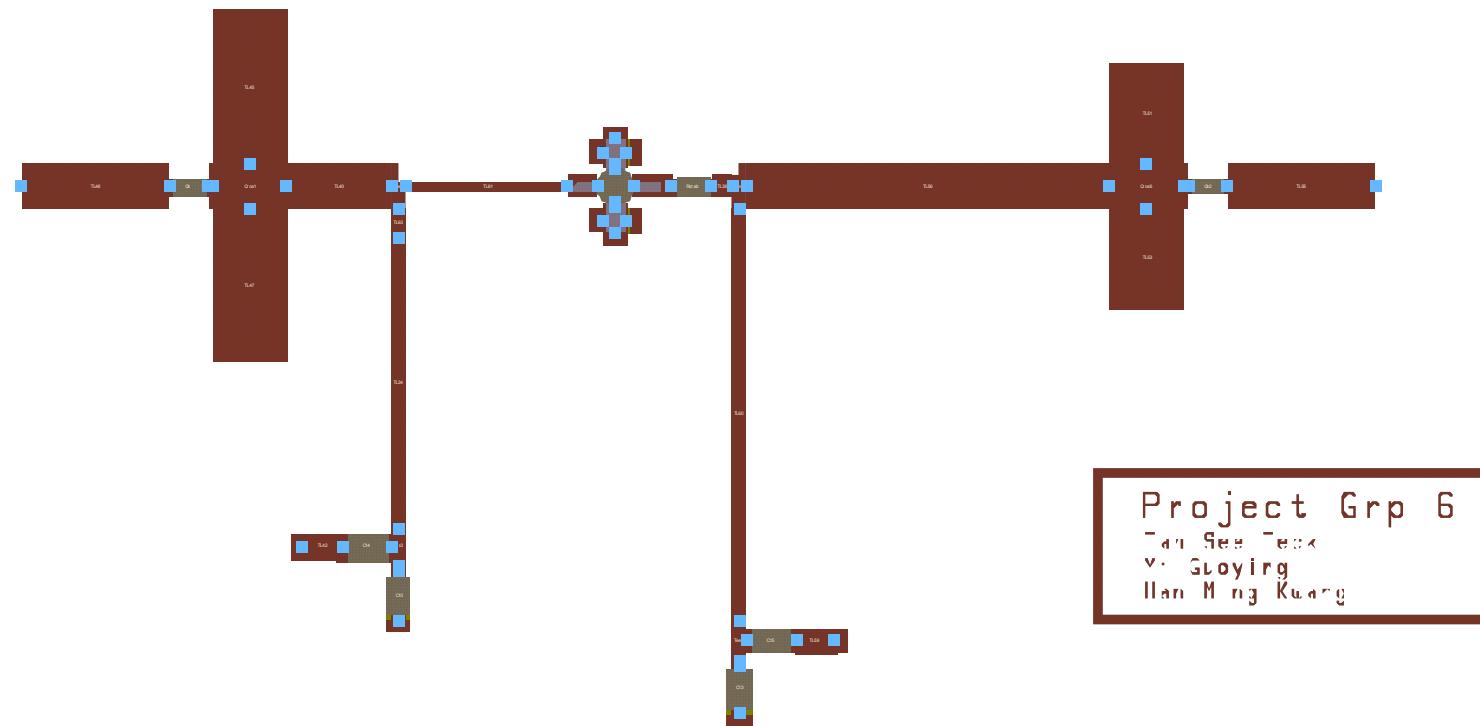
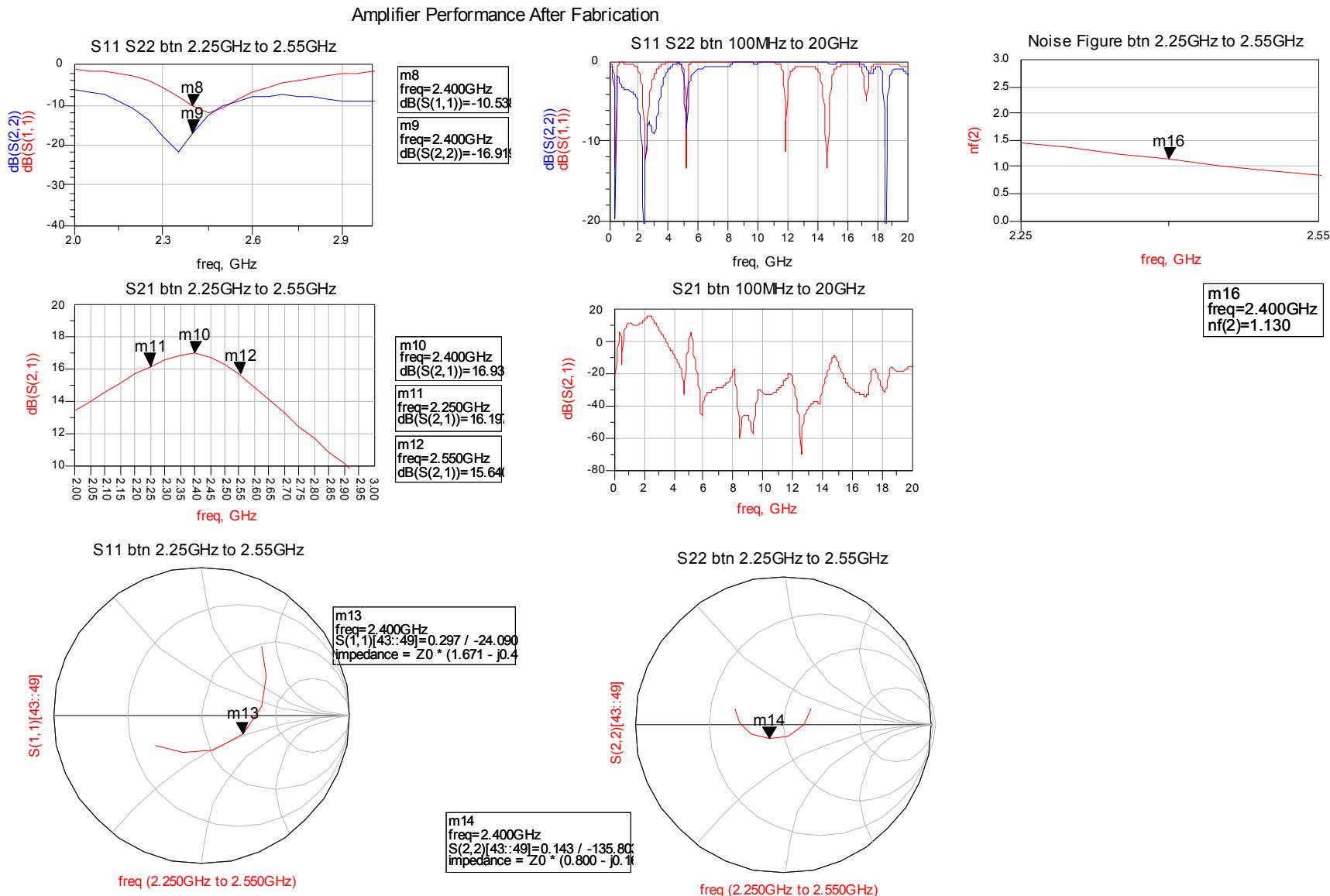


Figure 12 Resimulated Result using 33 ohm output stabilizing resistor

Appendix B shows the results from the fabricated amplifier design. We were unable to measure NF as the equipment is not available. Also due to the lack of exact value for the output stabilizing resistor, 33 ohm was chosen instead of the 30 ohm designed. Input stabilizing resistor of 36 ohm is also not soldered because no significant oscillation at low frequencies are observed.

Using the actual value of components used in the fabrication, the design is re-simulated and the result presented in Fig 12.

Comparison

	Simulated	Actual	Difference
S21	16.932 dB	16.191 dB	0.741 dB
S11	-10.538 dB	-11.997 dB	1.459 dB
S22	-16.919 dB	-15.134 dB	-1.785 dB

As expected output match is better than input match ($S22 < S11$). S21 has only 0.741 dB difference between actual and simulated.


Figure 13 Group 6 RF Amplifier 2.4GHz



Appendix B


26 Mar 2003 20:34:04

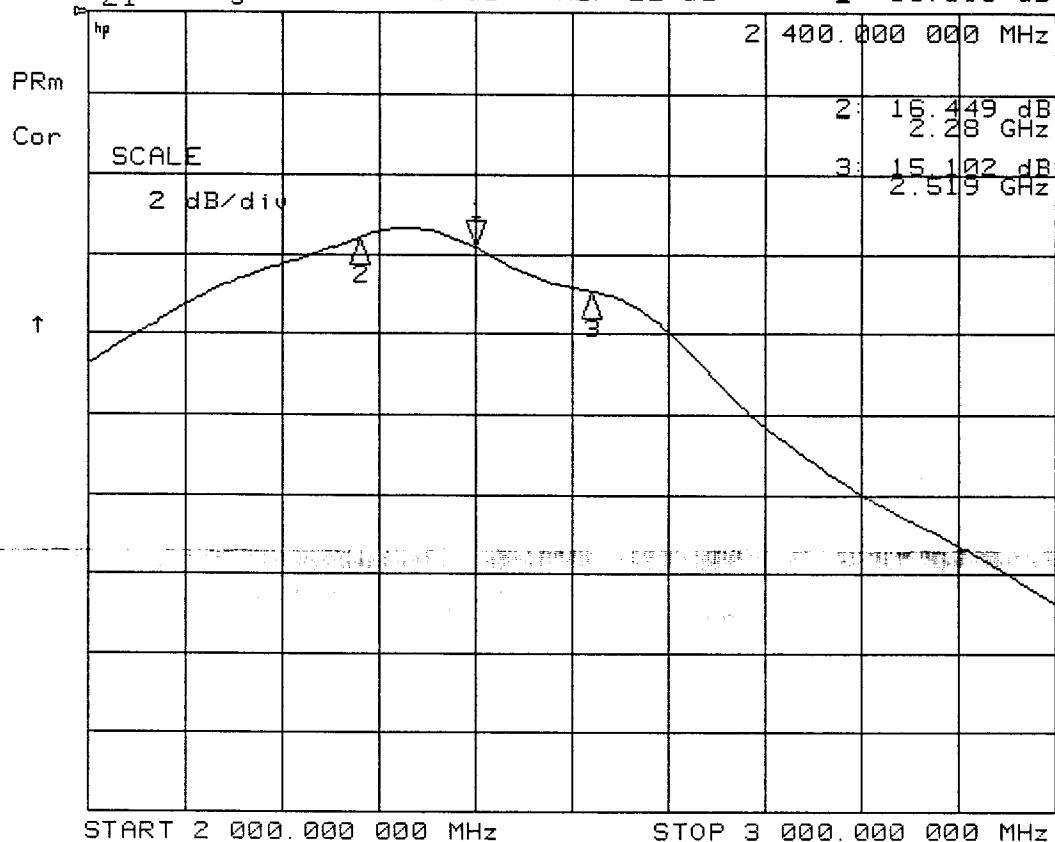CH1 S₂₁ Log MAG 2 dB/ REF 22 dB 1: 16.191 dB



26 Mar 2003 20:37:16

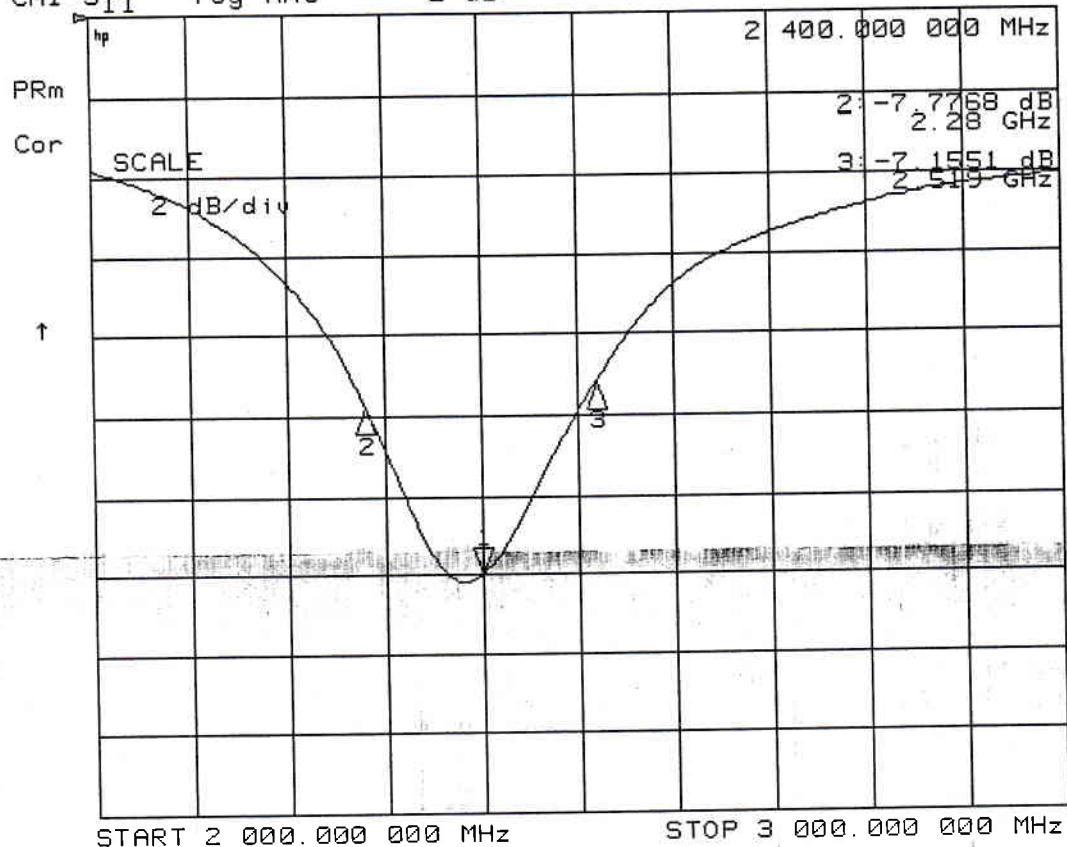CH1 S₁₁ Log MAG 2 dB/ REF 2 dB 1: -11.997 dB



26 Mar 2003 20:38:24


CH1 S₂₂ log MAG 5 dB/ REF 10 dB 1:-15.134 dB

22

Consequently, the GHG emissions from the energy sector are projected to decline by 1.1% per year between 2010 and 2050.

5 dB/dB 2.519 GHz

0 125, 476

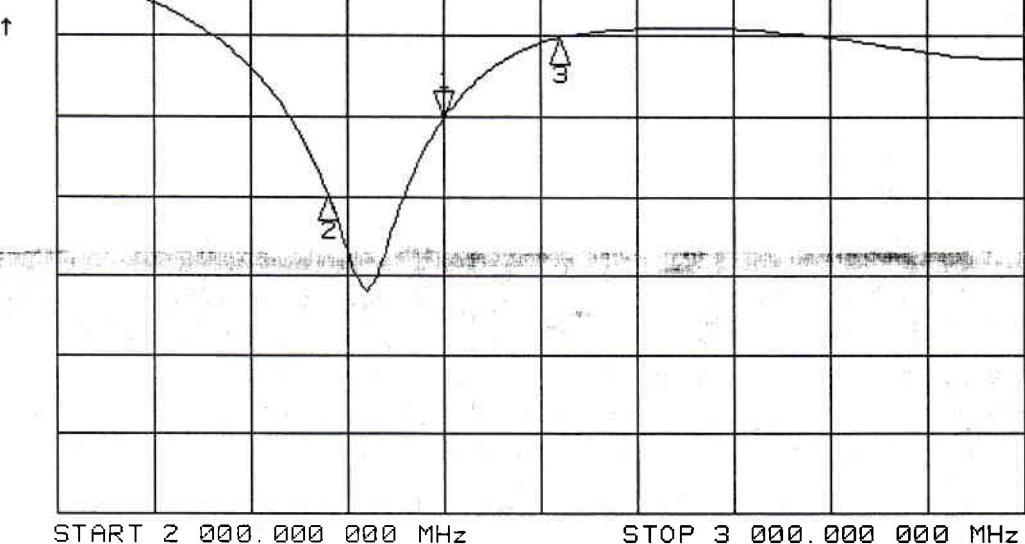

26 Mar 2003 20:36:32
CH2 S₁₂ Log MAG 5 dB/ REF -30 dB 1: -23.64 dB

