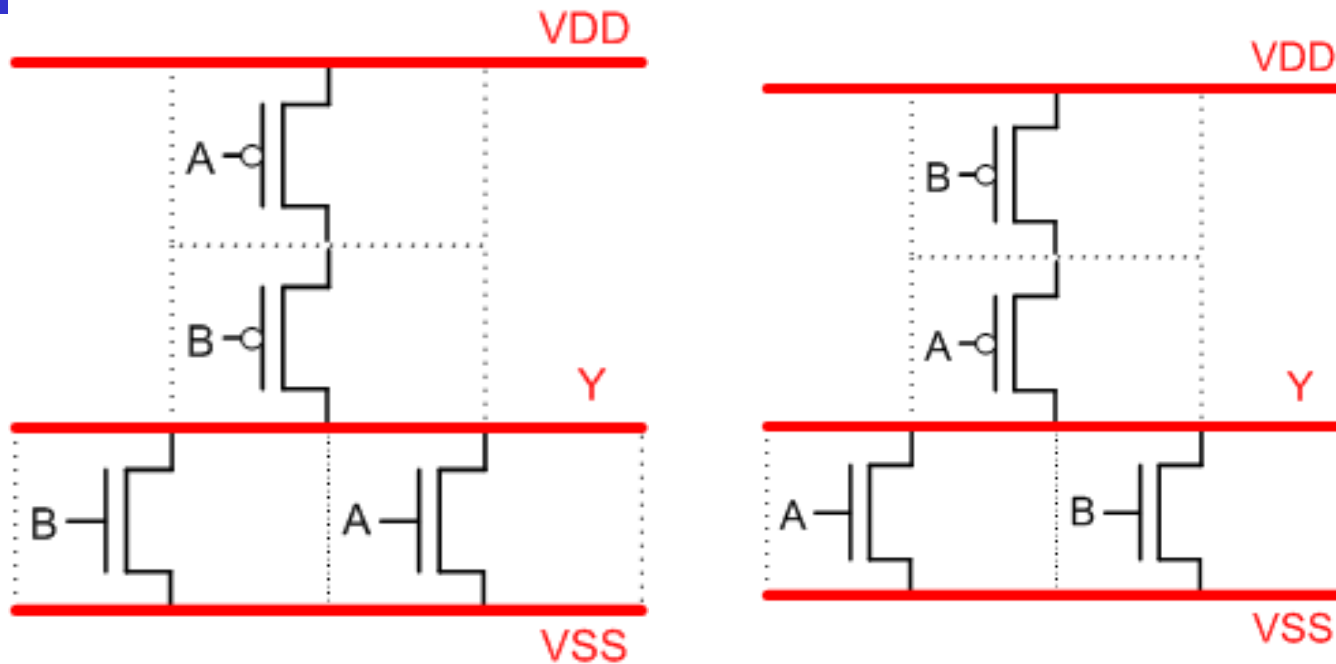


# NOR gate




2-input NOR gate.

**Note 1:** The order of inputs does not affect its logic equation.

$$Y = \overline{(A + B)}$$

# Multiple Inputs NOR

 


Note 2:

You can have more than 2 inputs. Similarly for NAND gate.

$$Y = \overline{(A + B)}$$

$$Y = \overline{(A + B + C)}$$

# NOR and NAND

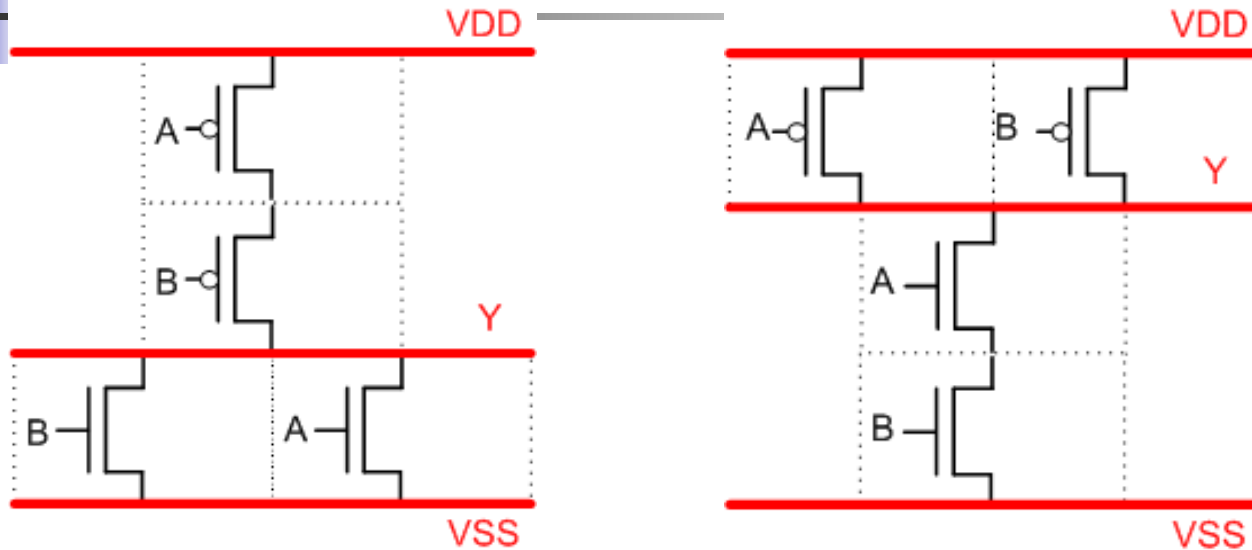

Note 3:

Top Part (divided by VOUT line) use PMOS and Bottom Part use NMOS.

Note 4: Duality.

If Top Part in series, Bottom Part in parallel.

If Bottom Part in series, Top Part in parallel.

Note 5:

NOR/OR is top series. NAND/AND is bottom series.

# DeMorgan's Theorems

You should know DeMorgan's Theorems:

Note 6:

$$\overline{(A + B)} = \overline{A} \cdot \overline{B}$$

$$\overline{(A \cdot B)} = \overline{A} + \overline{B}$$

You might need to manipulate the logic equation, before implementation of complex gate.


Conversion back and forth:

$$A + B = \overline{\overline{(A + B)}} = \overline{\overline{A} \cdot \overline{B}} = \overline{\overline{A}} + \overline{\overline{B}} = A + B$$


$$A \cdot B = \overline{\overline{(A \cdot B)}} = \overline{\overline{A} + \overline{B}} = \overline{\overline{A}} \cdot \overline{\overline{B}} = A \cdot B$$

# Example 1: $Y = \overline{A + BC}$

 
1. This is 2-input NOR  $\rightarrow$  top-series.



2.  $BC \rightarrow$  AND, bottom-series

 


3. Substitute with PMOS and NMOS

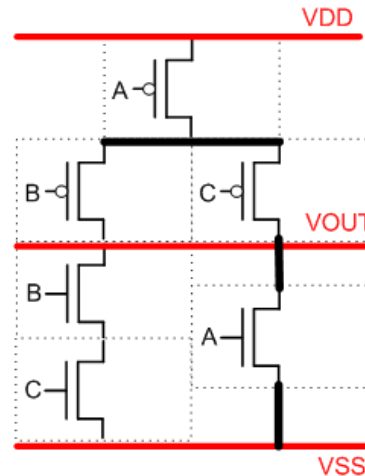


# Example 2: $Y = \overline{(A + BC + DE)}$

 
1. This is 3-input NOR  $\rightarrow$  top-series.



 2. **BC**  $\rightarrow$  bottom-series  
**DE**  $\rightarrow$  bottom-series




3. Substitute with PMOS and NMOS

 


4. Since substitution of MOS is straight forward, we will not focus on this from now on.

# Example 3: $Y = \overline{(A + B)C} + D$

 
1. This is 2-input NOR  $\rightarrow$  top-series.



 2.  $(A+B)C \rightarrow$  AND, bottom-series




3.  $(A+B) \rightarrow$  OR, top-series

 


# Example 4: $Y = \overline{(A + B) \cdot C \cdot (D + E)}$

 1. This is 3-input NAND  $\rightarrow$  bottom-series.



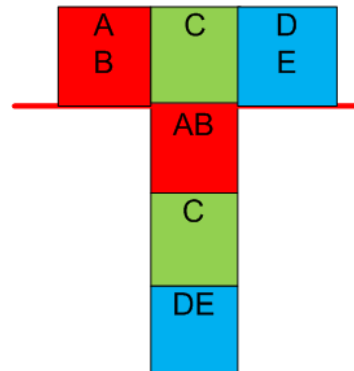
2.  $(A+B) \rightarrow$  OR, top-series  
 $(D+E) \rightarrow$  OR, top-series





# Example 5: $Y = \overline{\overline{A + B} \cdot (C + DE)}$

 
1. This is 2-input NAND  $\rightarrow$  bottom-series.



 2.  $\overline{A + B} = \overline{A} \cdot \overline{B} \rightarrow$  must be converted. AND, bottom-series

Note 8: Only AND or OR are allowed under the 1 big bar.

$$Y = \overline{\overline{A} \cdot \overline{B} \cdot (C + DE)}$$



3. Negated Inputs are allowed

# Example 6: $Y = \overline{\overline{AB} + (C + DE)}$



1.  $\overline{AB} = \overline{A} + \overline{B} \rightarrow$  must be converted.

Note 8: Only AND or OR are allowed under the 1 big bar.

2. This is 4-input NAND  $\rightarrow$  top-series.

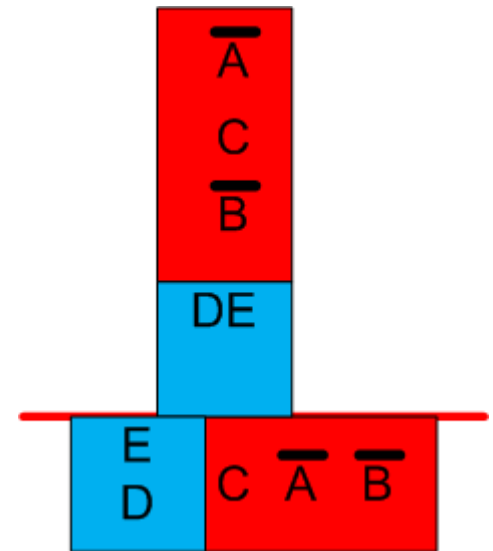 3.  $DE \rightarrow$  AND, bottom-series

$$Y = \overline{\overline{A} + \overline{B} + C + DE}$$



4. Order of inputs does not affect logic equation. Both solutions are acceptable


# Example 7: $Y = \overline{\overline{AB}} + (C + D)$

1. The equation is not in NAND or NOR form. You need to add 2 bars.

2. This is a 3-input NOR + INVERTER  $Y = \overline{\overline{AB} + C + D}$

 3.  $\overline{AB} = \overline{A} + \overline{B} \rightarrow$  OR, top series. must be converted.

**Note 8:** Only AND or OR are allowed under the 1 big bar.



3. You should draw the schematic of inverter

## Example 8: $Y = (A + B)(\bar{C} + \bar{D})$

1. The equation is not in NAND or NOR form. You need to add 2 bars.

2. This a 2-input NAND + INVERTER  $Y = \overline{(A + B)(\bar{C} + \bar{D})}$

