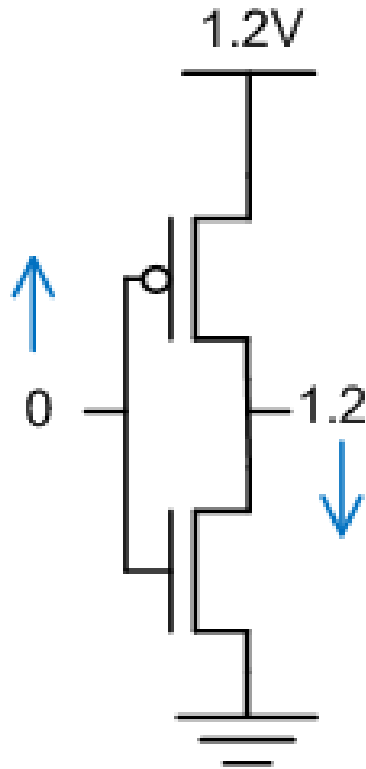



Inverter



As the input voltage rises from 0 to 1.2, the PMOS and NMOS will transit from one operation region to another. We are going to use V_{IN} rises from 0 to 1.2 for illustration.

So, what are the 5 operation region of inverter?

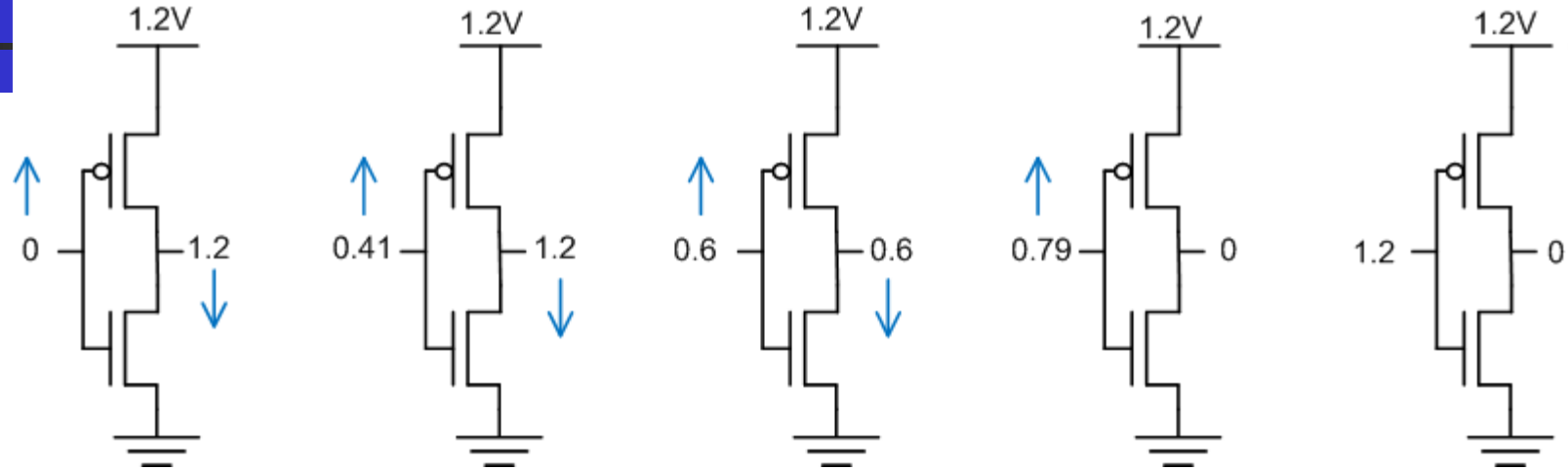As $V_{IN} \uparrow$, $V_{OUT} \downarrow$




Assume $V_{DD}=1.2V$, **threshold voltage** of PMOS and NMOS are $0.4V$.
 $|V_{thp}|=0.4V$ & $V_{thn}=0.4V$. || means magnitude or absolute (don't care about the sign).

There are 5 regions of operation as V_{IN} transits from $0V$ to $1.2V$ and V_{OUT} transits from $1.2V$ to $0V$.

We are not interested in the exact range of V_{IN} and V_{OUT} for each region. We just want to know that it does go through 5 regions of operation.

5 Regions?

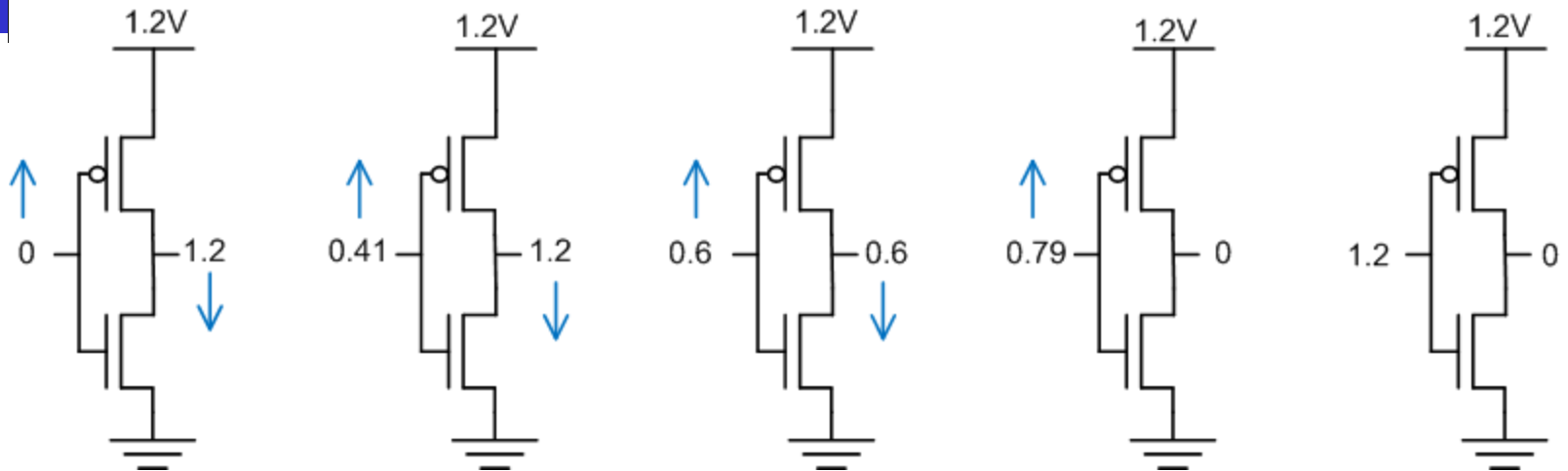

Operating Region	PMOS	NMOS
1	On, $ V_{gsP} > 0.4$	Off, $V_{gsN} < 0.4$
2	On	On, $V_{gsN} > 0.4$
3	On	On
4	On	On
5	Off, $ V_{gsP} < 0.4$	On



How many 'on'?

There are actually 2 regions of operation for MOS when it is on: **Linear** (act as a **small resistor**) and **Saturation** (act as a **current source**). So, we still have more work...

Let's go through each region one by one.

1st

PMOS:

$|V_{gs}| > |V_{th}| \rightarrow ||$ means absolute. Forget about the sign.

$1.2 > 0.4$ [on]

$|V_{ds}| < |V_{gs}| - |V_{th}|$



$0 < 1.2 - 0.4$ [Linear, Resistor]

NMOS:

$V_{gs} < V_{th}$

$0 < 0.4$ [off]

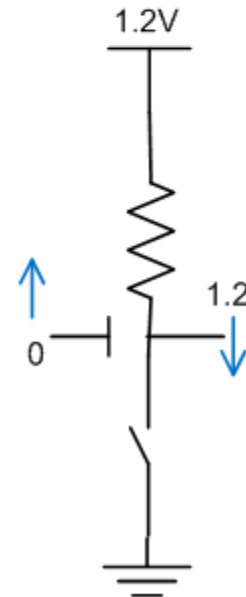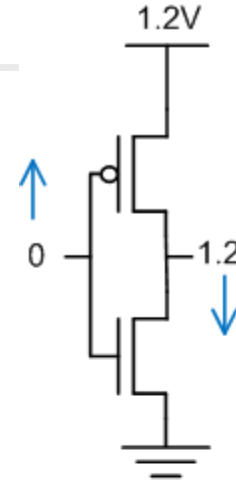There is no current flow through the resistor since there is not voltage drop across it.



2nd

PMOS:

$$|V_{gs}| > |V_{th}|$$

$$0.79 > 0.4 \text{ [on]}$$

$$|V_{ds}| < |V_{gs}| - |V_{th}|$$

$$0 < 0.79 - 0.4 \text{ [Linear, Resistor]}$$

NMOS:



$$V_{gs} > V_{th}$$

$$0.41 > 0.4 \text{ [on]}$$

$$V_{ds} > V_{gs} - V_{th}$$

$$1.2 > 0.41 - 0.4 \text{ [Saturation, Current Source]}$$

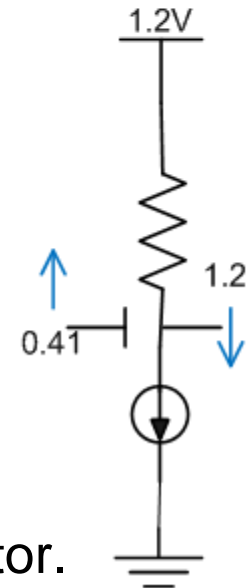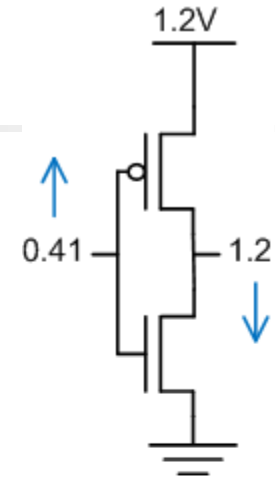VOUT will start to drop since current flow through resistor.



PMOS:

$$|V_{gs}| > |V_{th}|$$

$$0.6 > 0.4 \text{ [on]}$$

$$|V_{ds}| > |V_{gs}| - |V_{th}|$$

$$0.6 > 0.6 - 0.4 \text{ [Saturation, Current Source]}$$

NMOS:



$$V_{gs} > V_{th}$$

$$0.6 > 0.4 \text{ [on]}$$

$$V_{ds} > V_{gs} - V_{th}$$

$$0.6 > 0.6 - 0.4 \text{ [Saturation, Current Source]}$$

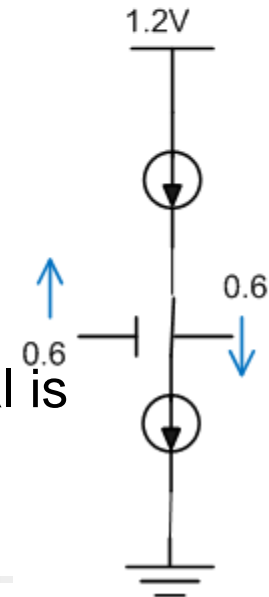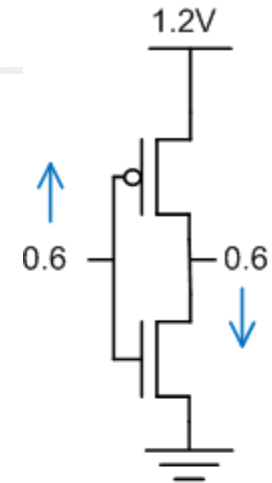Current flow directly from supply to ground. This interval is very short, or else power is wasted. V_{OUT} continues to drop.



PMOS:

$$|V_{gs}| > |V_{th}|$$

$$0.41 > 0.4 \text{ [on]}$$

$$|V_{ds}| > |V_{gs}| - |V_{th}|$$

$$1.2 > 0.41 - 0.4 \text{ [Saturation, Current Source]}$$

NMOS:



$$V_{gs} > V_{th}$$

$$0.79 > 0.4 \text{ [on]}$$

$$V_{ds} < V_{gs} - V_{th}$$

$$0 > 0.79 - 0.4 \text{ [Linear, Resistor]}$$

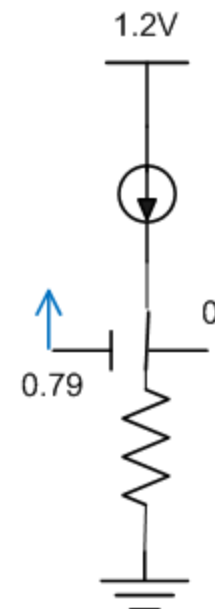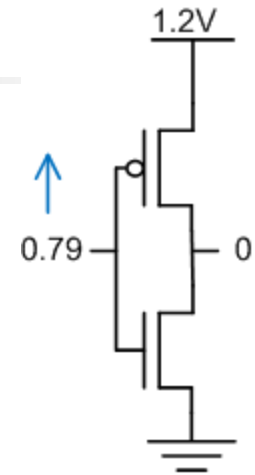The resistor will short VOUT to ground. Will the current flowing into resistor rises VOUT? **No**, current is small because PMOS size is not too large.



PMOS:

$$|V_{gs}| < |V_{th}|$$

$$0 < 0.4 \text{ [off]}$$

NMOS:



$$V_{gs} > V_{th}$$

$$1.2 > 0.4 \text{ [on]}$$

$$V_{ds} < V_{gs} - V_{th}$$

$$0 < 1.2 - 0.4 \text{ [Linear, Resistor]}$$

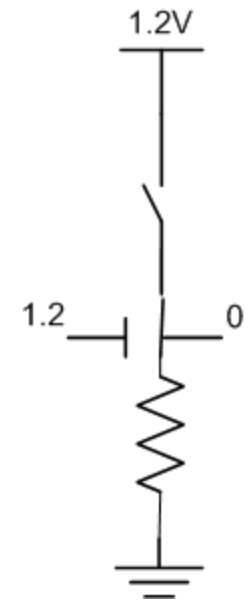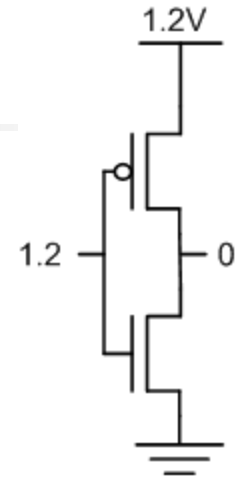No current flow through resistor since there is no voltage drop across it. V_{OUT} is always pull down to 0V.



Finally...

