

Lab 13: Digital Lab Revision

Objective:

* Digital Lab Revision

- a) From the 3-bit state machine state transition diagram shown in Figure 13.1, fill in the state transition table.

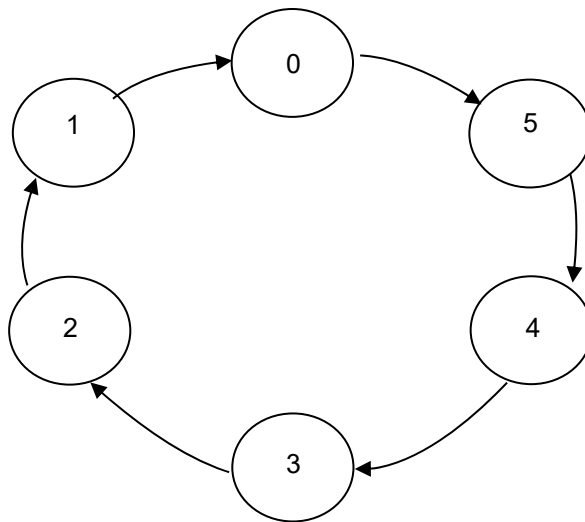


Figure 13.1 State Transition Diagram

Present State			Next State		
Q2	Q1	Q0	Q2*	Q1*	Q0*
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

Figure 13.2 State Transition table

b) D flip-flop is chosen to implement the state machine shown in Figure 13.1. Derive the equations for D2, D1 and D0 from Table 13.1.

		Q0	
		Q2Q1	Q0
		0	1
00			
01			
11			
10			

$Q2^* = D2 =$

		Q0	
		Q2Q1	Q0
		0	1
00			
01			
11			
10			

$Q1^* = D1 =$

		Q0	
		Q2Q1	Q0
		0	1
00			
01			
11			
10			

$Q0^* = D0 =$

- c) From the equations derived in b), create the schematic for the state machine shown in Figure 13.1.
 - (i) Print the schematic.
 - (ii) Write your **Login Account** on the printout.

- d) Perform simulation on this circuit.
 - (i) Set up the necessary forces for **CLK**
 - (ii) Run the simulation and print the waveform.
 - (iii) Write your **Login Account** on the printout