

Lab 4: Design of Digital Stop Watch (*decoder0to9*)


Objective:

* To design a Digital Stop Watch using concepts of digital system partitioning

Digital design – *decoder0to9*

Input				Output						
<i>q3</i>	<i>q2</i>	<i>q1</i>	<i>q0</i>	<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>g</i>
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1
1	0	1	0	X	X	X	X	X	X	X
1	0	1	1	X	X	X	X	X	X	X
1	1	0	0	X	X	X	X	X	X	X
1	1	0	1	X	X	X	X	X	X	X
1	1	1	0	X	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X	X

Table 4.1 *decoder0to9* Truth Table

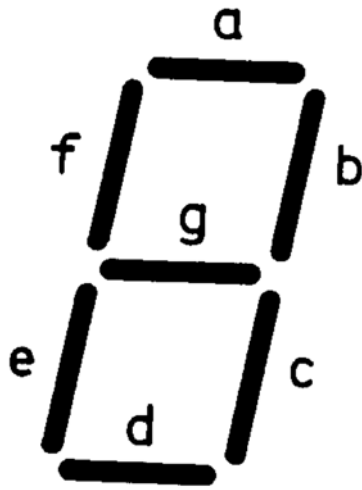

	Q1Q0	00	01	11	10
Q3Q2	00	1	0	1	1
01	0	1	1	1	
11	X	X	X	X	
10	1	1	X	X	

$$a = Q2Q0 + Q2BQ0B + Q3 + Q1$$

	Q1Q0	00	01	11	10
Q3Q2	00	1	1	1	1
01	1	0	1	0	
11	X	X	X	X	
10	1	1	X	X	

$$b = Q1Q0 + Q1BQ0B + Q2B$$

	Q1Q0	00	01	11	10
Q3Q2	00	1	1	1	0
01	1	1	1	1	
11	X	X	X	X	
10	1	1	X	X	

$$c = Q2 + Q1B + Q0$$

		Q1Q0			
		00	01	11	10
Q3Q2	00	1	0	1	1
	01	0	1	0	1
	11	X	X	X	X
	10	1	1	X	X

$$d = Q2Q1BQ0 + Q2BQ0B + Q2BQ1 + Q1Q0B + Q3$$

		Q1Q0			
		00	01	11	10
Q3Q2	00	1	0	0	1
	01	0	0	0	1
	11	X	X	X	X
	10	1	0	X	X

$$e = Q2BQ0B + Q1Q0B$$

		Q1Q0			
		00	01	11	10
Q3Q2	00	1	0	0	0
	01	1	1	0	1
	11	X	X	X	X
	10	1	1	X	X

$$f = Q2Q1B + Q2Q0B + Q1BQ0B + Q3$$

		Q1Q0			
		00	01	11	10
Q3Q2	00	0	0	1	1
	01	1	1	0	1
	11	X	X	X	X
	10	1	1	X	X

$$g = Q2BQ1 + Q2Q1B + Q1Q0B + Q3$$

Digital Stop Watch – *decoder0to9*

Reference Lab 3 to complete *decoder0to9*

1. Draw the *decoder0to9* circuit as shown in Figure 4.1.

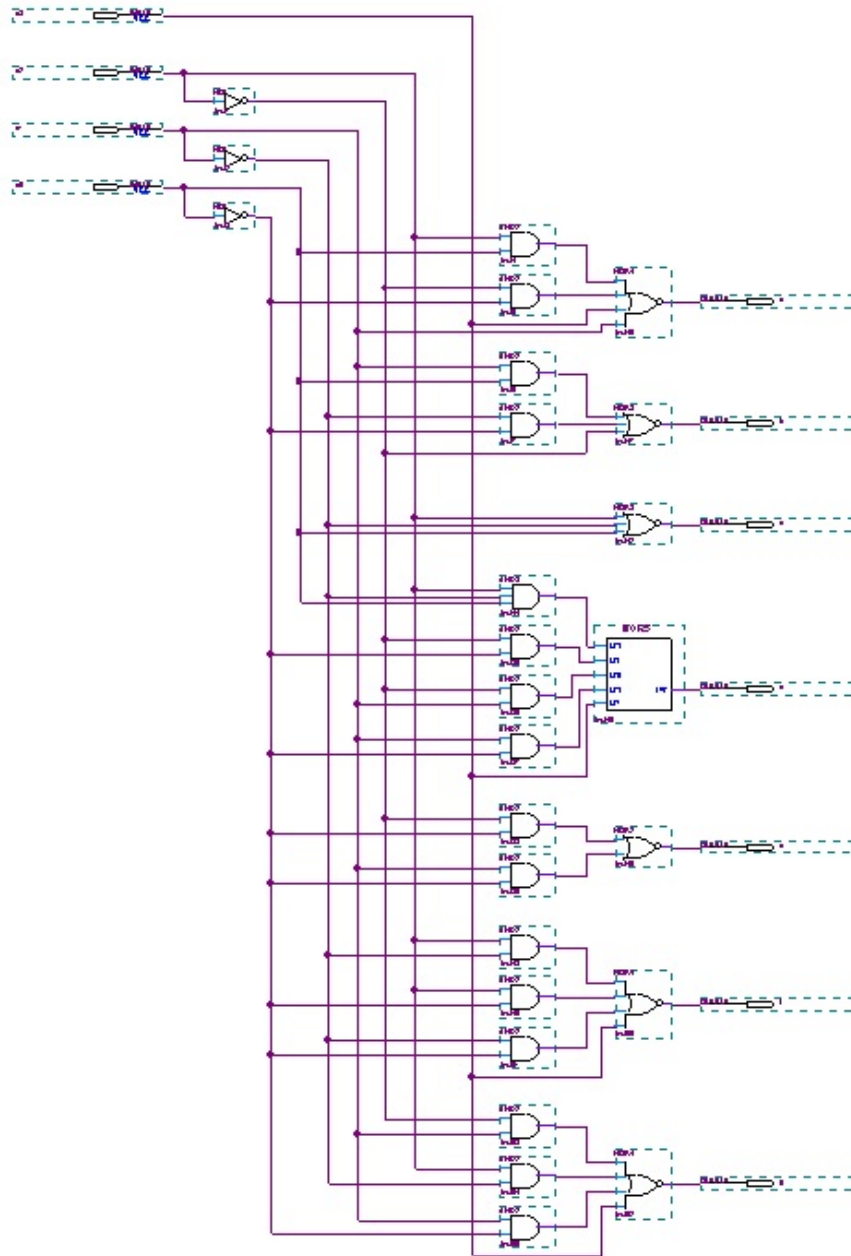


Figure 4.1 *decoder0to9* circuit

Symbols used: *and2*, *and3*, *nor2*, *nor3*, *nor4*, *nor5* and *not*

Pins used: *input* and *output*

Input pins names: *q3*, *q2*, *q1* and *q0*

Output pins names: *a*, *b*, *c*, *d*, *e*, *f* and *g*

2. Create symbol for the *decoder0to9* circuit and complete the circuit as shown in Figure 4.2 and Click **File > Save**. Compile the circuit and ensure no error. Ignore warning/s.

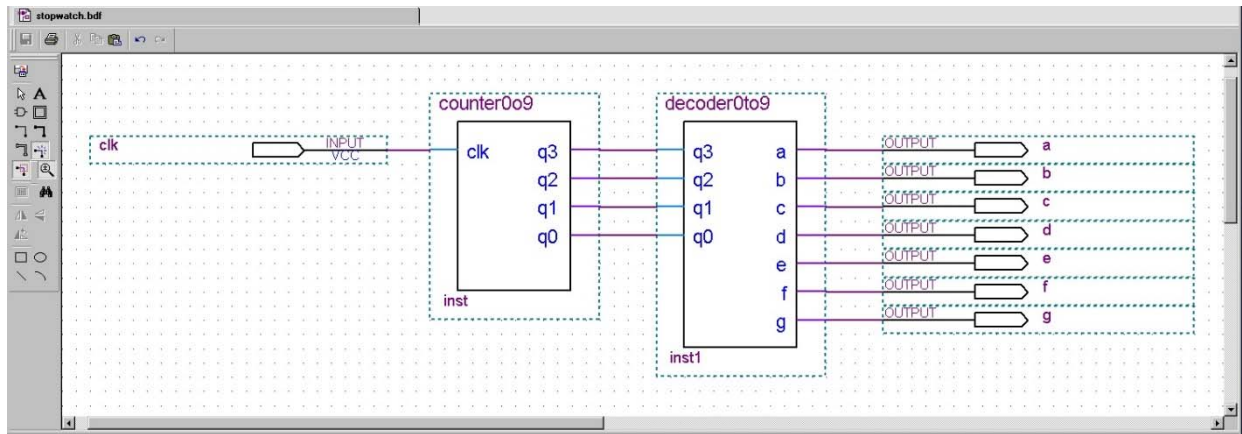


Figure 4.2 *stopwatch.bdf* with *counter0to9* and *decoder0to9* symbols connected

3. Update/edit the stopwatch Vector Waveform File – *stopwatch.vwf* to test the *decoder0to9* circuit as shown in Figure 4.3. (Refer to Lab 1 if you have forgotten how to create/edit Vector Waveform File).

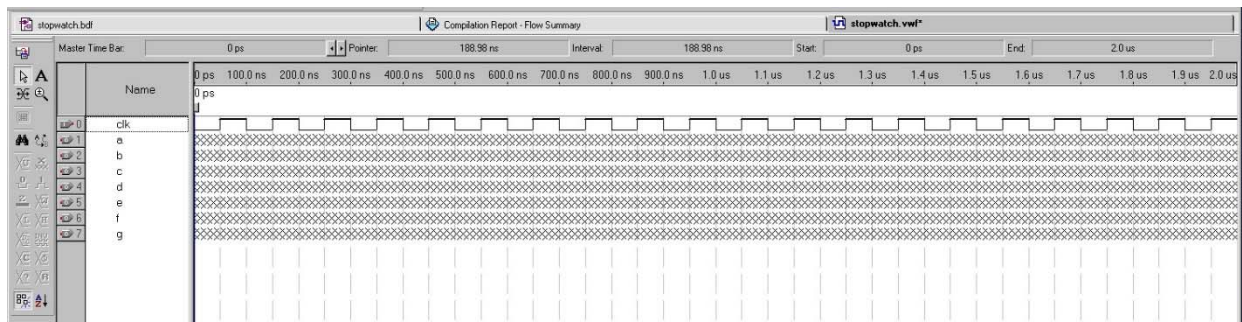


Figure 4.3 *stopwatch* Vector Waveform File to test *decoder0to9*

4. Simulate the circuit to obtain the results as shown in Figure 4.4. Verify the *decoder0to9* outputs using Table 4.2.

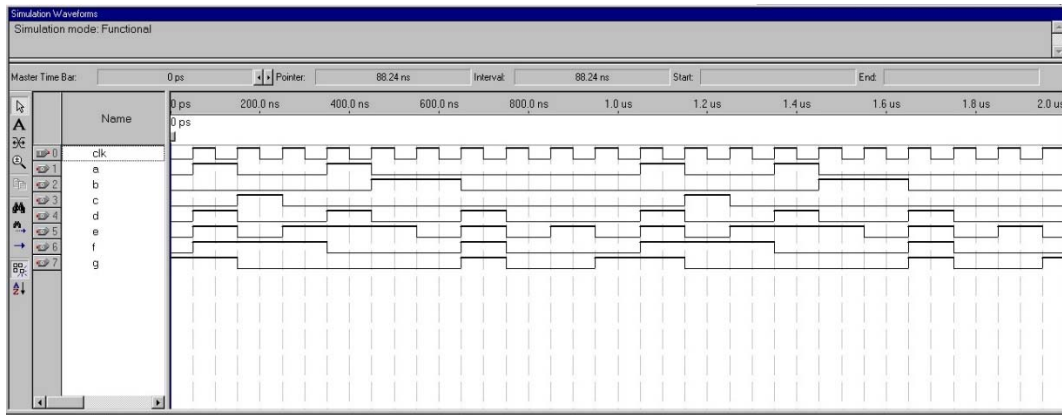


Figure 4.4 stopwatch (*decoder0to9*) waveform

<i>Count</i>	<i>0</i>	<i>1</i>	<i>2</i>	<i>3</i>	<i>4</i>	<i>5</i>	<i>6</i>	<i>7</i>	<i>8</i>	<i>9</i>
<i>Time</i>	<i>0ns</i>	<i>100ns</i>	<i>200ns</i>	<i>300ns</i>	<i>400ns</i>	<i>500ns</i>	<i>600ns</i>	<i>700ns</i>	<i>800ns</i>	<i>900ns</i>
<i>a</i>	0	1	0	0	1	0	0	0	0	0
<i>b</i>	0	0	0	0	0	1	1	0	0	0
<i>c</i>	0	0	1	0	0	0	0	0	0	0
<i>d</i>	0	1	0	0	1	0	0	1	0	0
<i>e</i>	0	1	0	1	1	1	0	1	0	1
<i>f</i>	0	1	1	1	0	0	0	1	0	0
<i>g</i>	1	1	0	0	0	0	0	1	0	0

Table 4.2 Expected *decoder0to9* outputs